

ECEN405 Lab 4 Report

Boost Converter

Niels Clayton : 300437590
Lab Partner: Nickolai Wolfe

1 Boost Converter Calculations

Calculate output voltage V_{out} for:
 $V_{in} = 20V$
 $D = 0.333$

$$\begin{aligned} V_{out} &= \frac{1}{1-D} V_{in} \\ &= \frac{1}{1-0.333} 20 \\ &= 30V \end{aligned}$$

Calculate the output current I_{out} for:
 $R_L = 500\Omega$

$$\begin{aligned} I_{out} &= \frac{V_{out}}{R_L} \\ &= \frac{30}{500} \\ &= 0.06A \end{aligned}$$

Calculate the inductor current ripple I_{Δ} for:
 $I_{ripple} = 20\%$

$$\begin{aligned} I_{delta} &= I_{ripple} \cdot I_{out} \cdot \frac{V_{out}}{V_{in}} \\ &= 0.2 \cdot 0.06 \cdot \frac{30}{20} \\ &= 0.018A \end{aligned}$$


Calculate the switching frequency f_s for:
 $L = 4mH$

$$\begin{aligned} f_s &= \frac{V_{in} (V_{out} - V_{in})}{L \cdot I_{\Delta} \cdot V_{out}} \\ &= \frac{20 (30 - 20)}{0.004 \cdot 0.018 \cdot 30} \\ &= 92,592Hz \end{aligned}$$

Calculate the output voltage ripple V_{Δ} :

$$\begin{aligned} I_{outmax} &= I_{out} + \left(\frac{I_{\Delta}}{2} \right) \\ &= 0.06 + \left(\frac{0.018}{2} \right) \\ &= 0.069 \\ V_{\Delta} &= \frac{I_{outmax} \cdot D}{f_s \cdot C} \\ &= \frac{0.069 \cdot 0.333}{92592 \cdot 100\mu} \\ &= 0.002484 \end{aligned}$$


2 Low Side MOSFET Drain Voltage

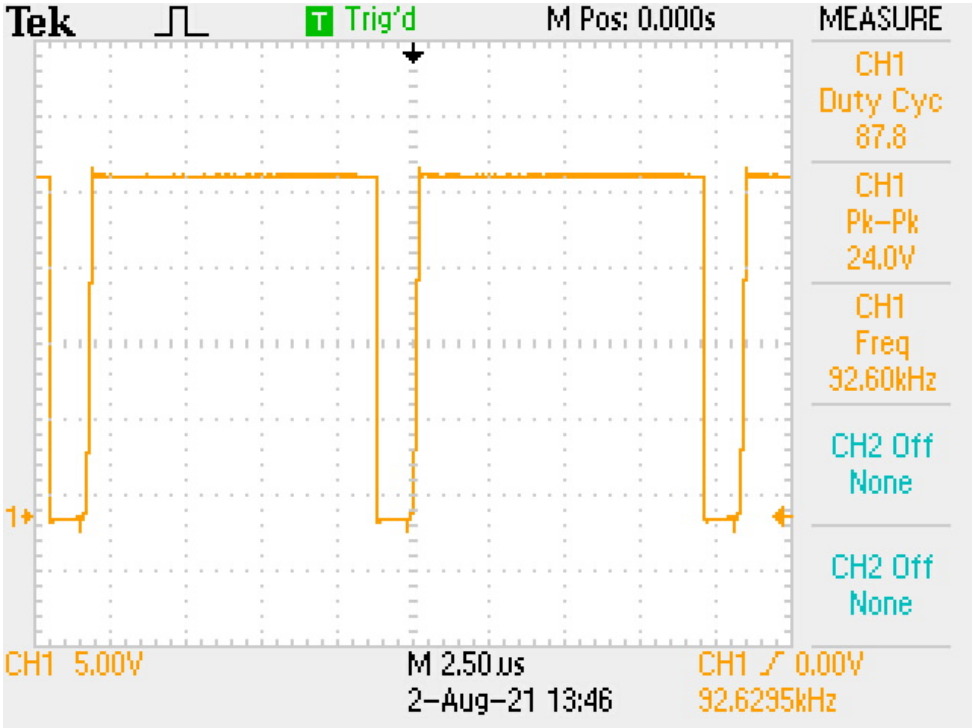

Low Side MOSFET Drain Voltage From Oscilloscope with a 10% duty cycle

From the image above we can see that the voltage at the drain of the low side MOSFET has been scaled to be larger than the 5V control signal. We can also see that the 10% duty cycle has been inverted, giving a 90% duty cycle. This is due to the MOSFET pulling the voltage at the drain to ground when switched on. We are also able to see that there is very little ringing on the output signal, with very little over and undershoot. Finally it can be seen that the falling edge of the voltage waveform is very sharp, however the rising edge as a slight slope to it, this is most likely due to us visualising the charging curve of the capacitor.

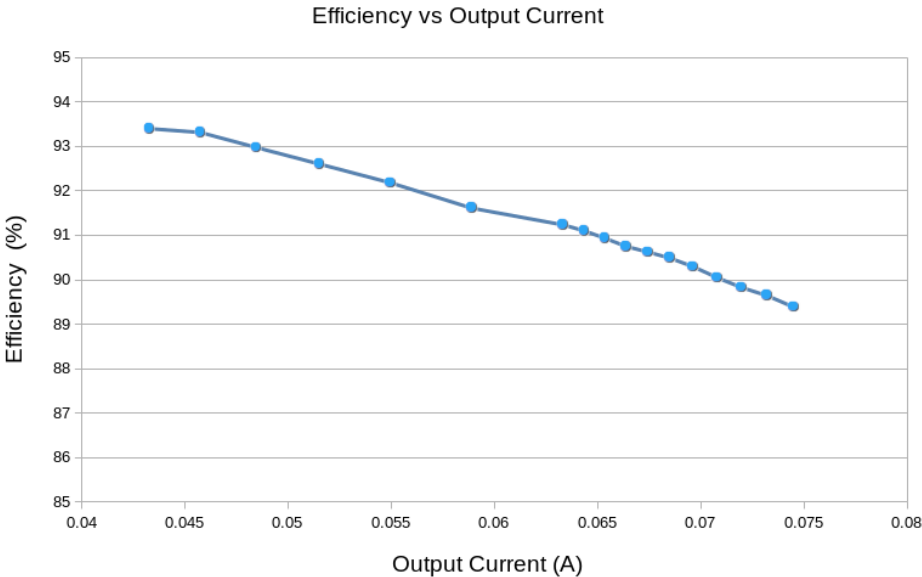3 Boost Converter Efficiency vs Output Current



Boost Converter Efficiency Plot