

# Feedback Control Design in Regulated DC Power Supplies


- Peak-Current-Mode Control

1



1

## Voltage feedback - Summary

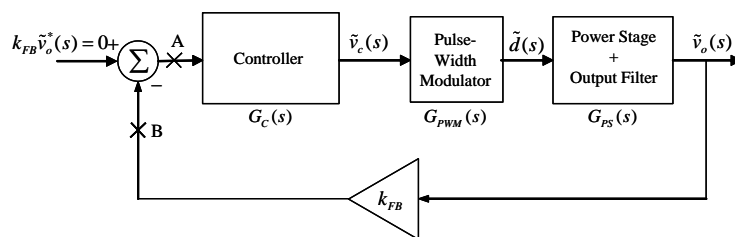

$$G_c(s) = \frac{k_c}{s} \frac{(1 + s/\omega_z)^2}{(1 + s/\omega_p)^2}$$

2



2

### Three General Amplifier types

Type 1

Type 3

Type 2

3

3

### PEAK-CURRENT MODE CONTROL

- Peak-Current-Mode Control, and
- Average-Current-Mode Control. ← In PFC Lecture

4

4

## Current Mode Control

- Difference I mode vs V mode
  - Current mode has **two feedback loops**; one to control the inductor current, the other to control the capacitor (output) voltage
  - Control system can be same as V mode; but for practical reasons, in inner loop, controlling the inductor current acts to remove its effect in the power stage.
  - Hence no resonant tank to worry about.
  - So only a single pole of output cap at high frequencies

5



5

## Limitation of Current Mode


- Sense a current using a resistor (CT going to a resistor)
- Feed it into PWM IC
- However as load current decreases the magnitude of the signal must naturally decrease.
- If load is light the current signal will be negligible and the current feedback loop has no effect on the system. So, **current mode control becomes voltage mode control at light loads.**

6



6

## RHPZ

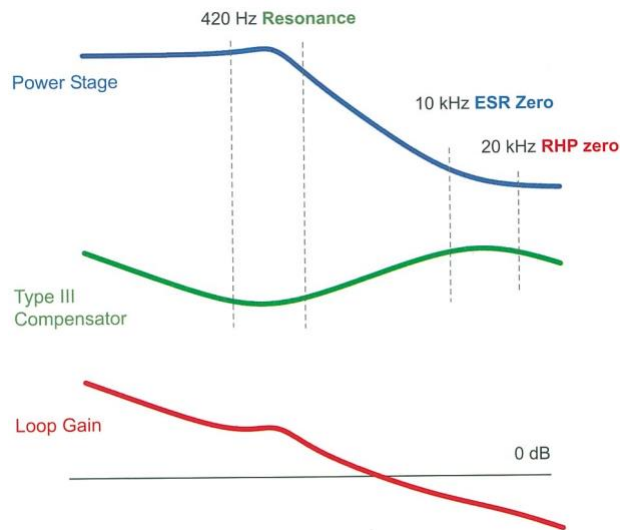

7



7

## Solutions?


- Bandwidth of the converter to be designed such that RHPZ occurs at much higher frequencies than the bandwidth
- Beware that zeros moves with loads
- I mode Compensator design:
  - First pole at origin
  - Zero at  $1/5$  the selected crossover frequency
  - Second pole at ESR zero of cap or RHP Zero whichever is lower



8
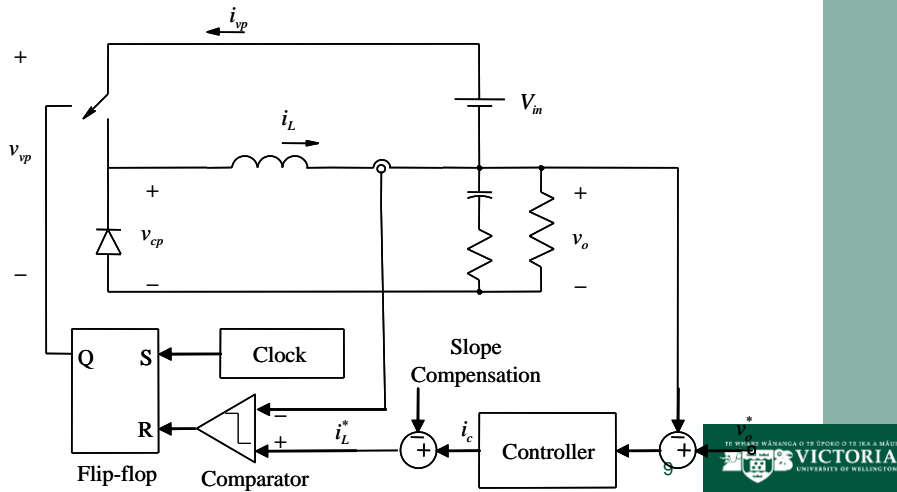
## PEAK-CURRENT MODE CONTROL

- Peak-Current-Mode Control, and
- Average-Current-Mode Control.




9

## Slope Compensation


- When the duty cycle of the current mode converter exceeds 50%, the converter will oscillate at a subharmonic of the switching frequency
- Similar to the effect of RHP zero effect but at subharmonics
- This happens when we try to compare average inductor current and the dc value of the sampled inductor current.

10


10

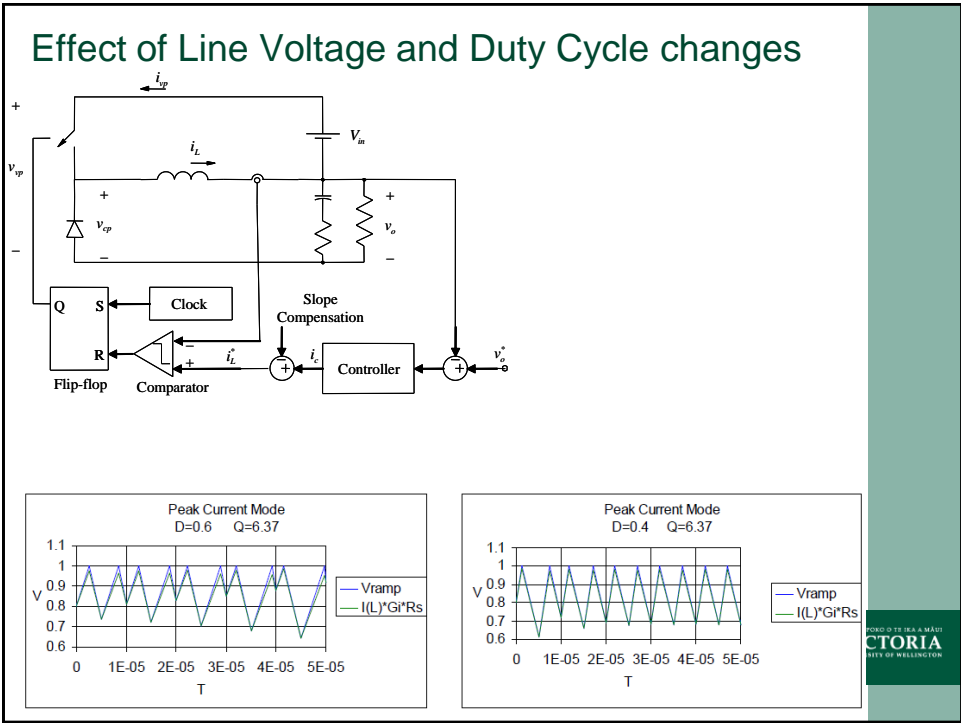


11

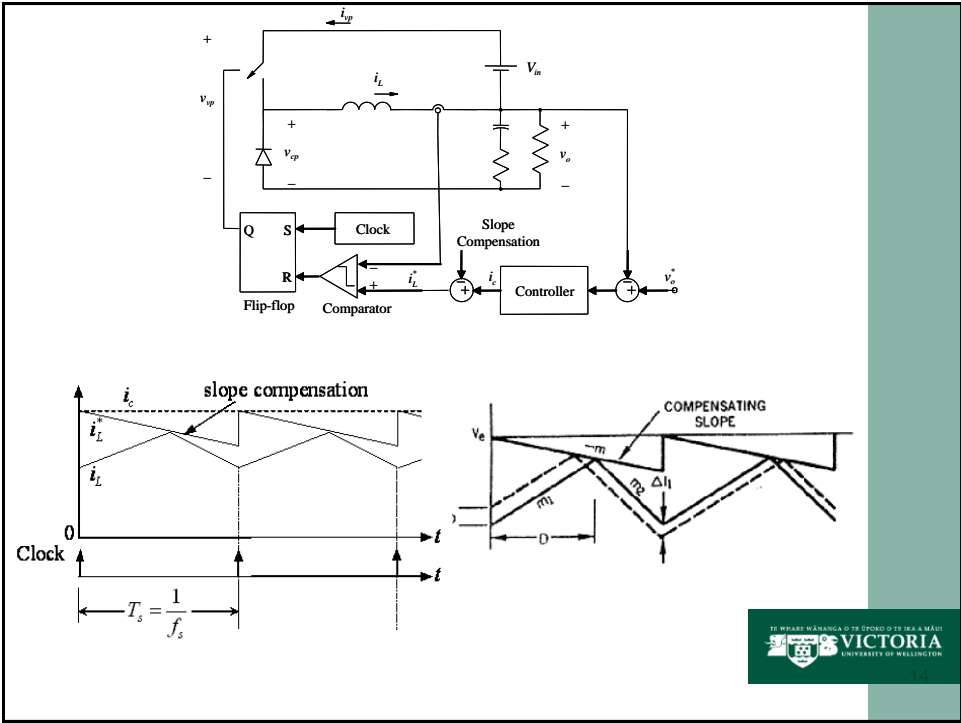


14

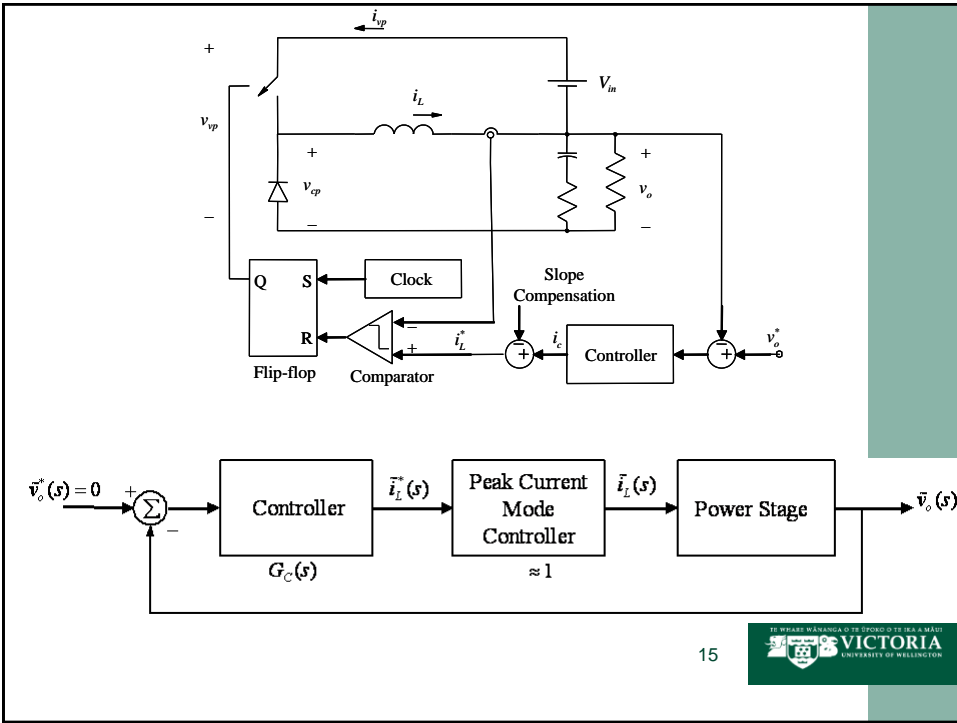


15

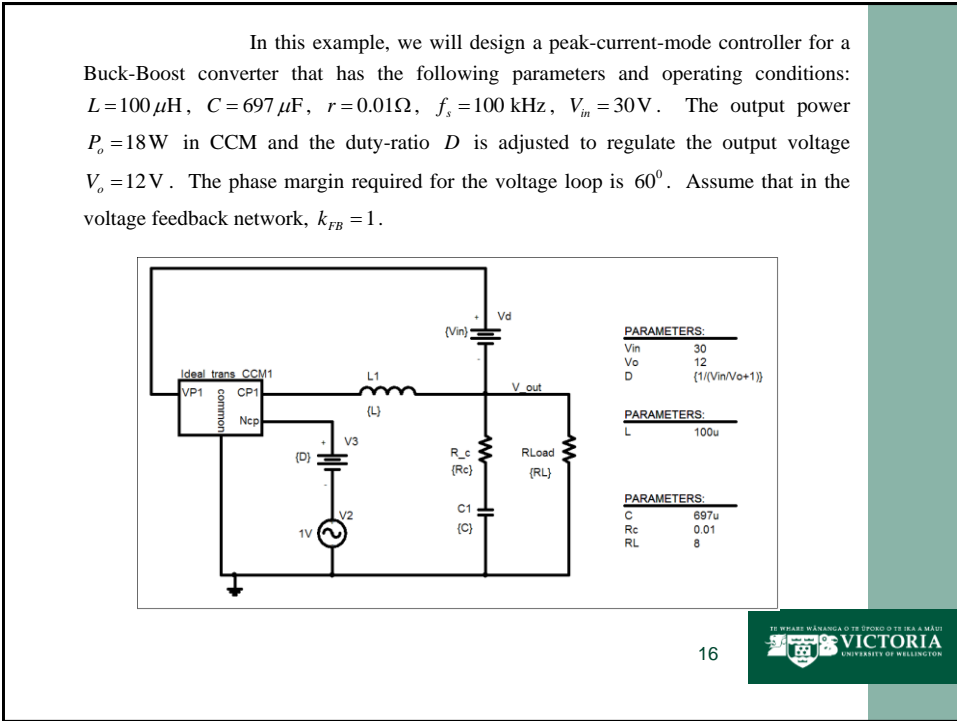

16

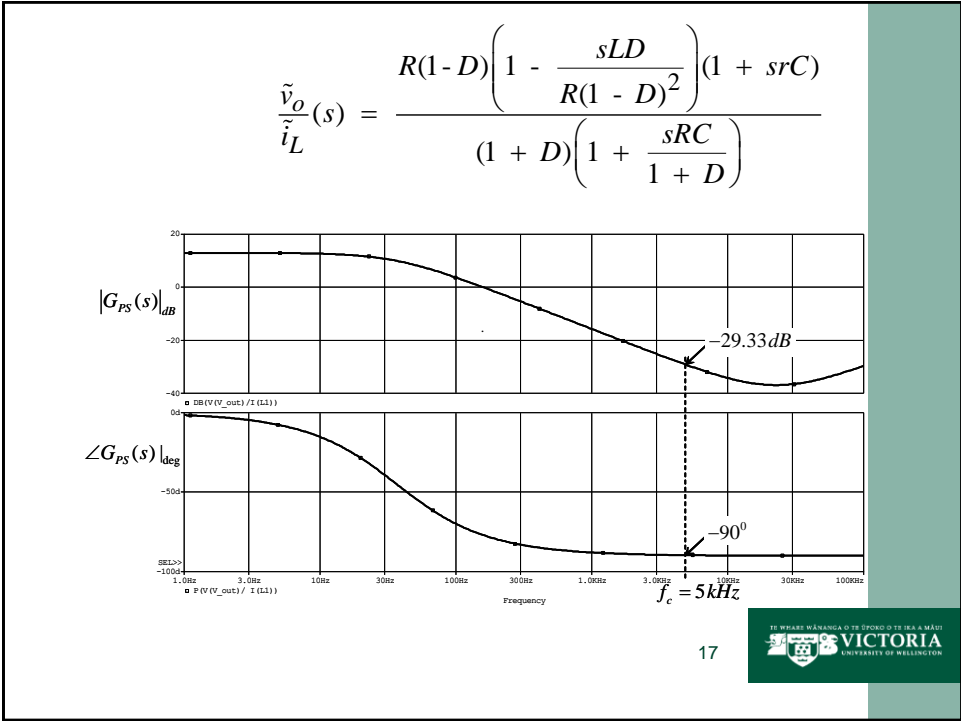


17

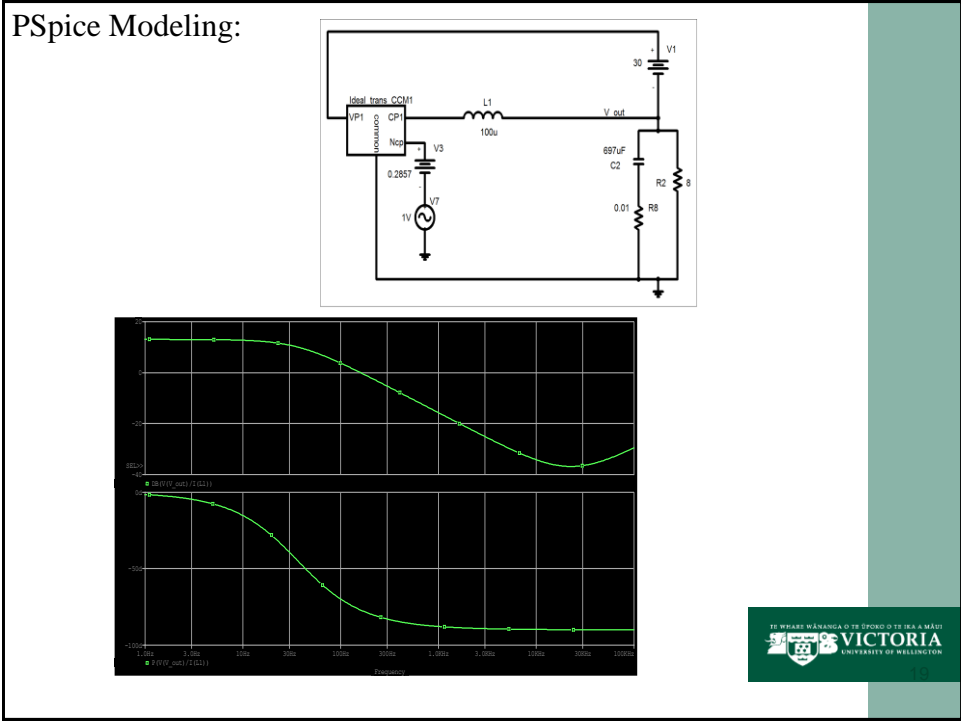

19



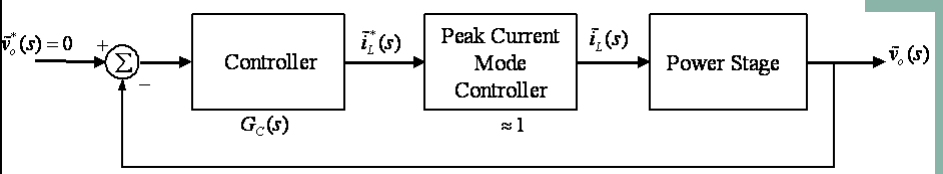

$$G_c(s) = \frac{k_c}{s} \frac{(1 + s/\omega_z)}{(1 + s/\omega_p)} \quad f_c = \sqrt{f_z f_p} \quad \sqrt{\frac{f_p}{f_z}} = \tan\left(45^\circ + \frac{\phi_{boost}}{2}\right)$$


$$|G_c(s)|_{f_c} \times |G_{PS}(s)|_{f_c} = 1$$

All other equations from voltage mode are valid

20

TE WHARE WĀNANGA O TE IPONGO O TE IKA A MĀUI  
VICTORIA  
UNIVERSITY OF WELLINGTON

20

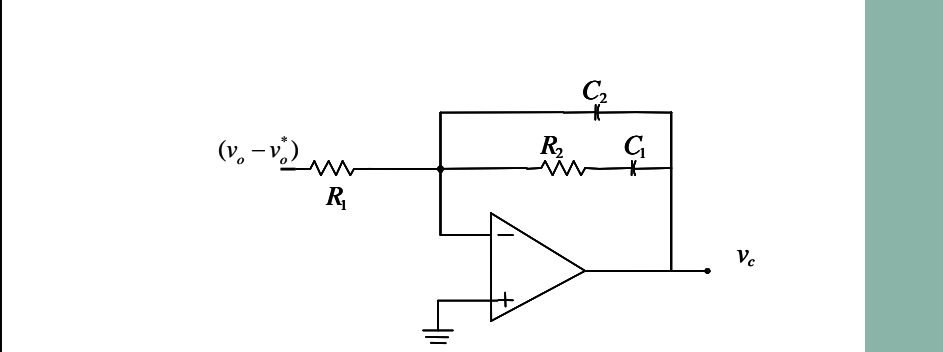

$$R_1 = 10\text{ k}\Omega$$

$$C_2 = \frac{\omega_z}{\omega_p R_1 k_c} = 30\text{ pF}$$


$$C_1 = C_2 (\omega_p / \omega_z - 1) = 380\text{ pF}$$

$$R_2 = 1/(\omega_z C_1) = 315\text{ k}\Omega$$

21

TE WHARE WĀNANGA O TE IPONGO O TE IKA A MĀUI  
VICTORIA  
UNIVERSITY OF WELLINGTON

21

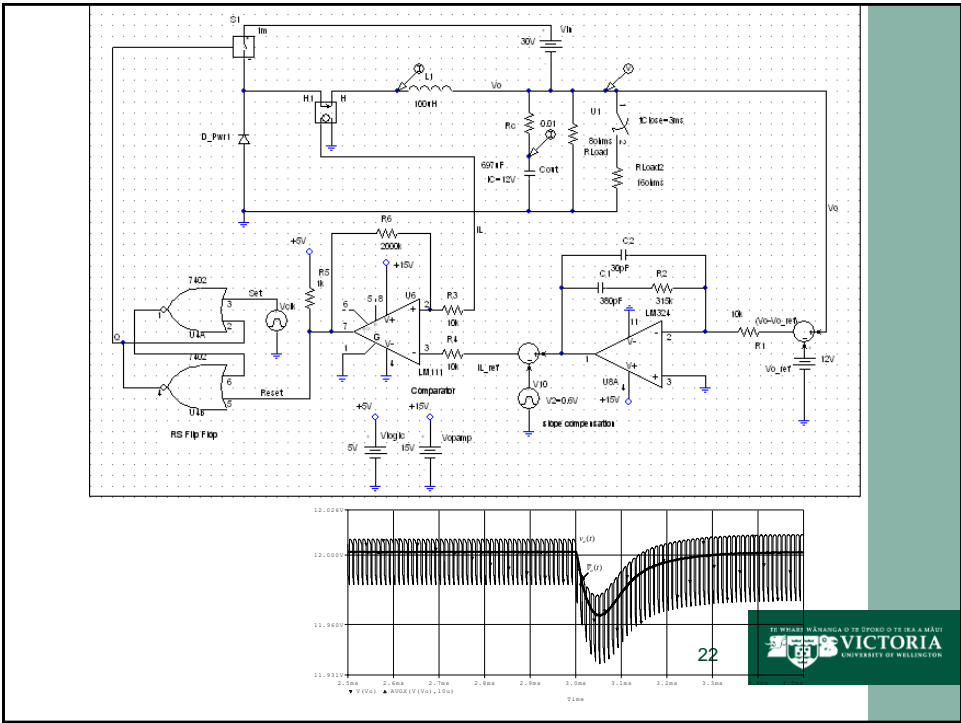

22

# Summary

## Feedback Control Design in Regulated DC Power Supplies

- RHP Zero
- Peak-Current-Mode Control


25

25

## Concept Quiz

The crossover frequency in the peak-current-mode control can be selected to be higher than that in the voltage-mode control, because of the phase angle of the power stage in the control block-diagram below?

- A. True
- B. False

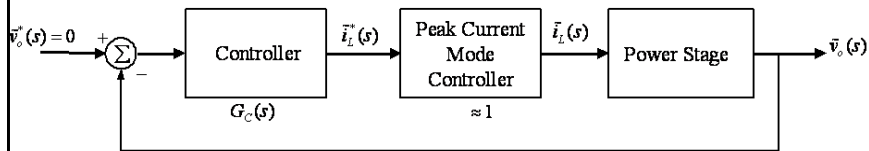

26