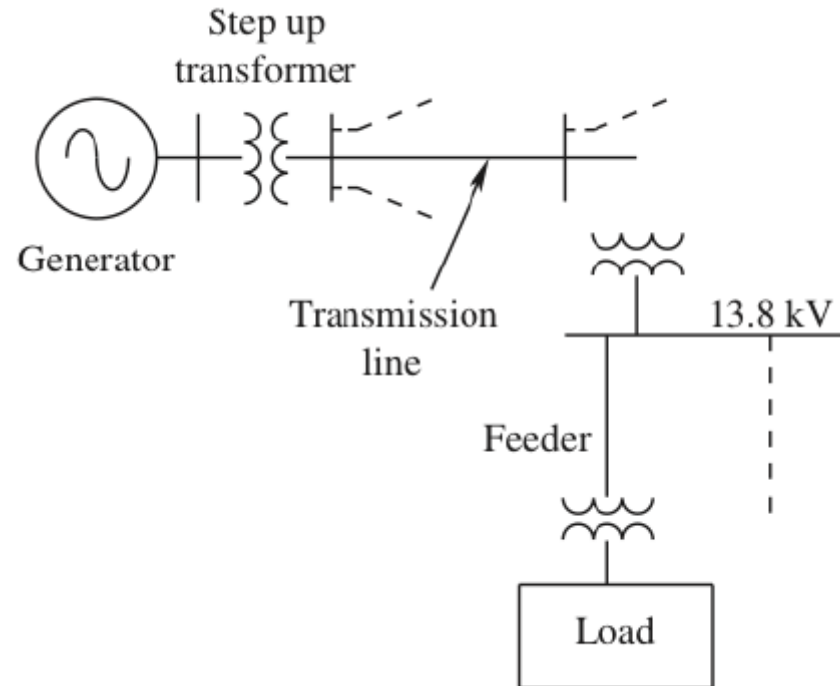



# EEEN313/ECEN405

## **Three Phase Power 2 with examples**

# 3 phase single line diagram





# Per-phase circuit

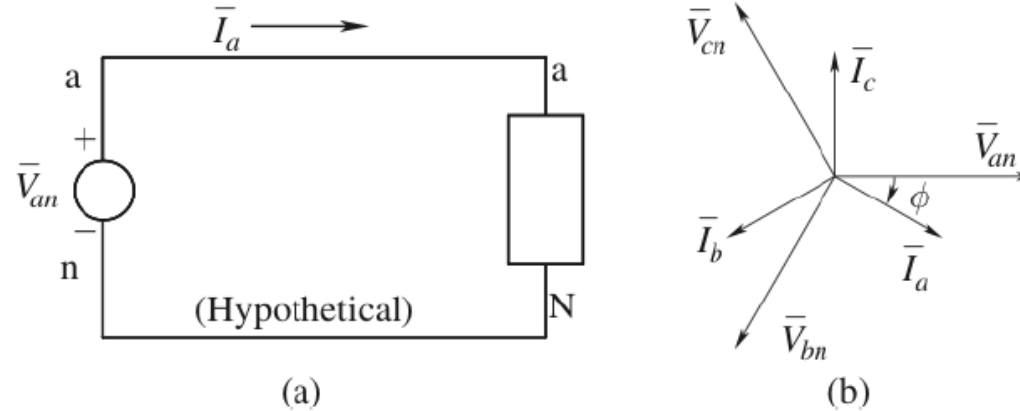

The total real and reactive powers in a balanced three-phase circuit can be obtained by multiplying the per-phase values by a factor of three.  
The power factor is same as its per-phase value.

# Mutual coupled phases

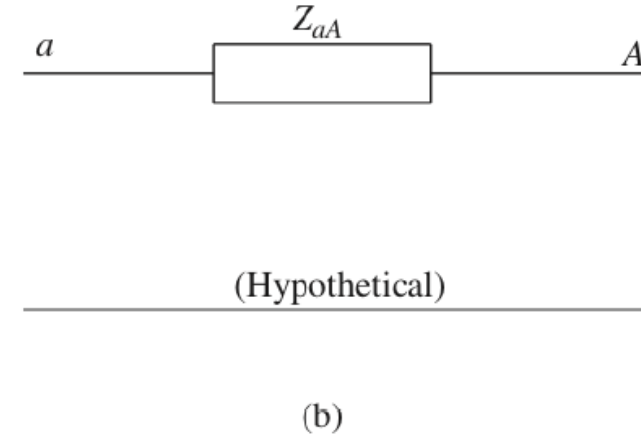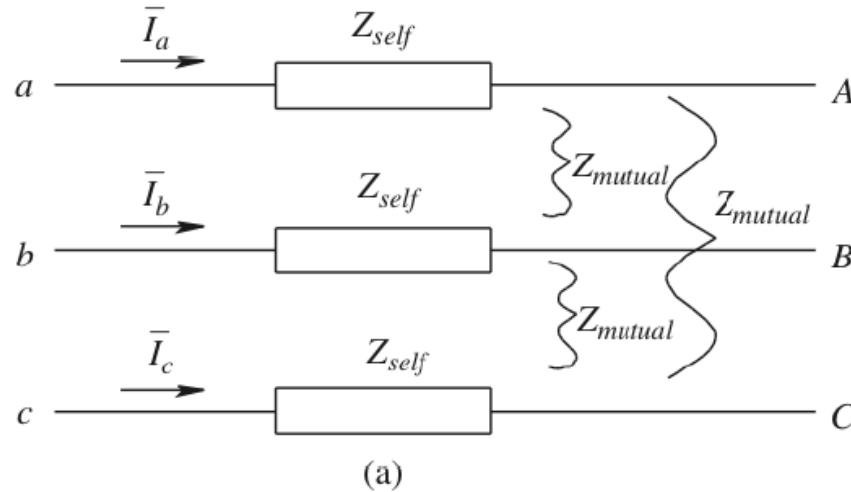


$$\bar{V}_{aA} = Z_{self}\bar{I}_a + Z_{mutual}\bar{I}_b + Z_{mutual}\bar{I}_c$$

$$\bar{I}_a + \bar{I}_b + \bar{I}_c = 0. \quad \bar{V}_{an} + \bar{V}_{bn} + \bar{V}_{cn} = 0 \quad \text{and} \quad v_{an}(t) + v_{bn}(t) + v_{cn}(t) = 0$$

$$\bar{V}_{aA} = (Z_{self} - Z_{mutual})\bar{I}_a = Z_{aA}\bar{I}_a \quad \text{where} \quad Z_{aA} = Z_{self} - Z_{mutual}$$

# Line-Line voltages

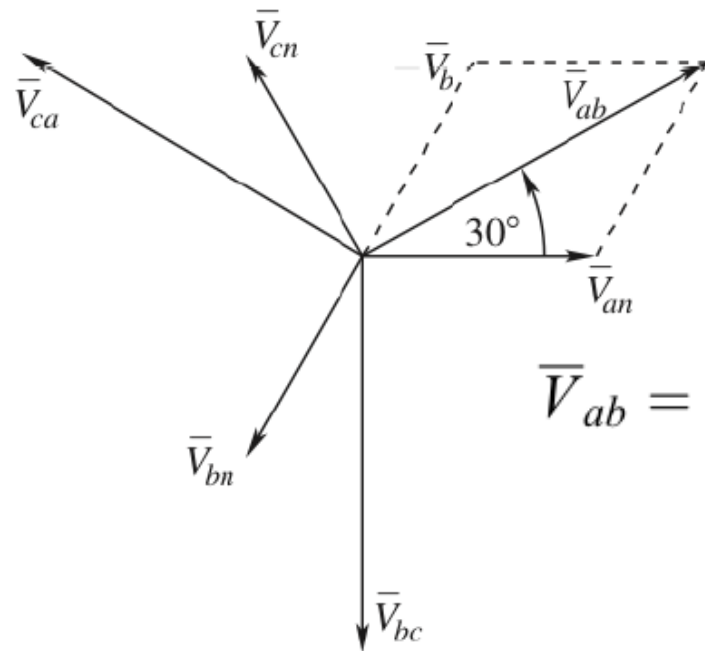

$$\bar{V}_{ab} = \sqrt{3}V_{ph} \angle \frac{\pi}{6}$$

$$\bar{V}_{bc} = \sqrt{3}V_{ph} \angle \left( \frac{\pi}{6} - \frac{2\pi}{3} \right) = \sqrt{3}V_{ph} \angle -\frac{\pi}{2}$$

$$\bar{V}_{ca} = \sqrt{3}V_{ph} \angle \left( \frac{\pi}{6} - \frac{4\pi}{3} \right) = \sqrt{3}V_{ph} \angle -\frac{7\pi}{6}$$

$$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{bn}, \quad \bar{V}_{bc} = \bar{V}_{bn} - \bar{V}_{cn}, \quad \text{and} \quad \bar{V}_{ca} = \bar{V}_{cn} - \bar{V}_{an}$$

$$V_{LL} = \sqrt{3}V_{ph} \quad \bar{V}_{ab} \text{ leads } \bar{V}_{an} \text{ by } \pi/6 \text{ radians } (30^\circ).$$

# Example 1

- A 460-volt, 50-hertz three-phase Y-connected load draws a line current of  $65\angle -26^\circ$  A.
- Find P, Q, and S for this three-phase load

$$P = \sqrt{3}|V_{line}||I_{line}| \cos \theta = \sqrt{3}(460)(65)\cos(0^\circ - (-26^\circ))$$
$$= 46.55 \text{ kW}$$

$$Q = \sqrt{3}|V_{line}||I_{line}| \sin \theta = \sqrt{3}(460)(65)\sin(0^\circ - (-26^\circ))$$
$$= 22.70 \text{ kVAR}$$

I've chosen  $0^\circ$  as the angle for the specified load voltage.

$$S = P + jQ = 46.5 + j22.70 \text{ kVA}$$
$$= 51.79\angle 26^\circ \text{ kVA}$$

## Example 2

Another three-phase system operates at 8,100 volts and 50 hertz. The connected load absorbs 285 kW at 0.85 power factor lagging. Find the line current.


$$\begin{aligned} P &= \sqrt{3} |V_{line}| |I_{line}| pf \\ I_{line} &= \frac{P}{\sqrt{3} |V_{line}| pf} \angle -\cos^{-1}(pf) \\ &= \frac{285 \times 10^3}{\sqrt{3} (8100) (0.85)} = 23.9 \angle -31.8^\circ \text{ A} \end{aligned}$$

We have to consciously insert the correct sign into the phase angle.

Here, the power factor is *lagging* so the load must be inductive. That means that the current *lags* the voltage so its angle must be negative relative to the angle of the voltage
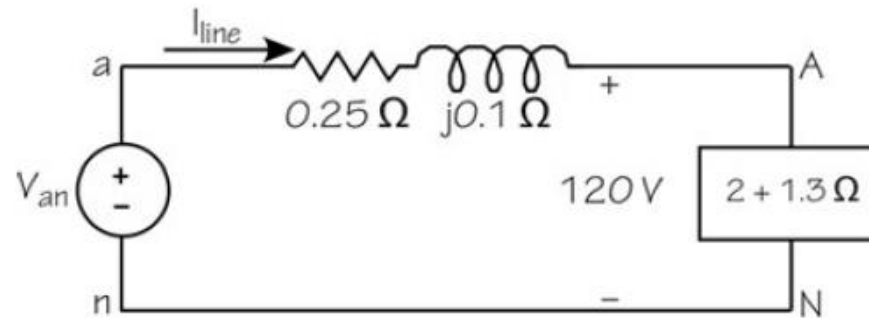
## Example 3 – Y connected

A 208-V, 60-Hz, 3 $\phi$ , Y-connected load has a per-phase impedance of  $2 + j1.3 \text{ } \Omega$ . The wire impedance is  $0.25 + j0.1 \text{ } \Omega$ . Find the line current, the power factor of the load, and the percent efficiency of the system.



The line current, in both the single-phase equivalent and the three-phase system, is the load voltage (taken with a phase angle of  $0^\circ$ ) divided by the load impedance:

$$I_{line} = \frac{120}{2 + j1.3} = 50.3 \angle -33.0^\circ \text{ A}$$

The power factor of the load comes from the phase angle of the load voltage (chosen as  $0^\circ$ ) and the phase angle of the line current

$$pf = \cos(-33.0^\circ) = 0.839 \text{ lagging}$$




The power absorbed by the single-phase load is

$$P_{load} = (120)(50.3)(0.839) = 5.06 \text{ kW}$$

$$P_{loss} = (0.25)(50.3)^2 = 632.5 \text{ W}$$
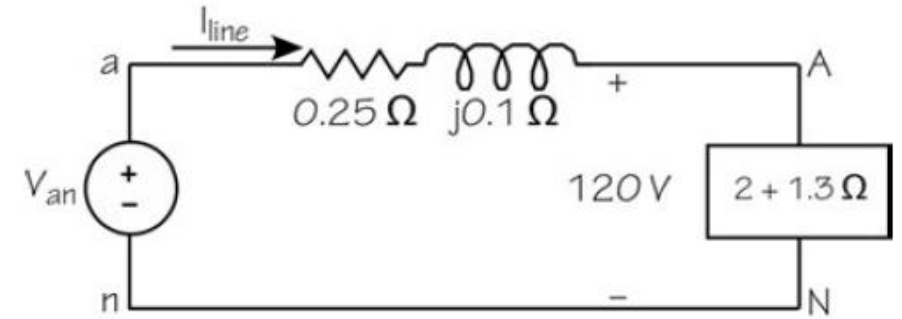
$$\% \eta = 100 \frac{5.06 \times 10^3}{5.06 \times 10^3 + 632.5} = 88.9\%$$



## Example 4 – Delta connected Load

$$I_{line} = \frac{120}{0.667 + j0.433} = 150.9 \angle -33.0^\circ \text{ A}$$


$$P_{load} = (120)(150.9)(\cos(-33.0^\circ)) = 15.19 \text{ kW}$$

This result is exactly three times that for the Y-connected impedance.

$$P_{loss} = (0.25)(150.9)^2 = 5.69 \text{ kW}$$

$$\% \eta = 100 \frac{15.19}{15.19 + 5.69} = 72.7\%$$

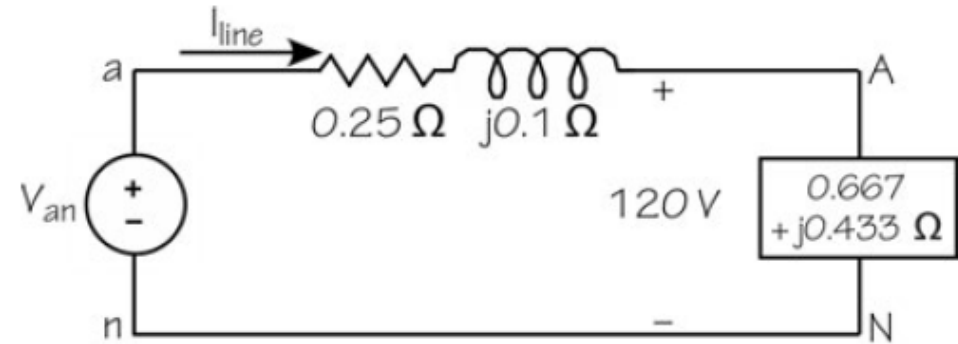The efficiency is low because the wiring is not large enough to efficiently carry the large current.




## Example 5 – Three Phase Motor

A three-phase 2400-volt, 250-horsepower induction motor is 85% efficient. Its rated power factor is 83%. The line impedance is  $1.6 + j0.56$  ohms per phase. Find the overall efficiency of the system

$$P_{motor} = \frac{250 \times 746}{0.85} = 219.4 \text{ kW}$$
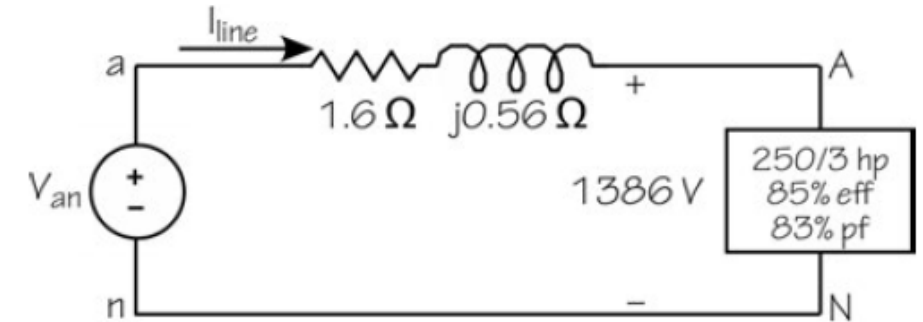
$$V_{load} = \frac{2400}{\sqrt{3}} = 1386 \text{ V} \quad (\text{single phase equivalent})$$



$$P_{motor/phase} = 219.4/3 = 73.14 \text{ kW @0.83 lagging}$$

$$\% \eta = 100 \frac{73.14}{73.14 + 6.47} = 91.9\% \quad (\text{electrical})$$

$$I_{line} = \frac{73.14 \times 10^3}{(1386)(0.83)} \angle -\cos^{-1}(0.83) = 63.58 \angle -33.9^\circ \text{ A}$$

$$\text{overall } \% \eta = 0.919 \times 0.85 = 78.1\%$$

$$P_{loss/phase} = (1.6)(63.58)^2 = 6.47 \text{ kW}$$

(electrical and motor)

## Example 6 – Power Factor Support for Three Phase Motor

How much reactive power do we need to maintain a power factor of 0.9?

$$Q_{load / phase} = 73.14 \tan(\cos^{-1}(0.83)) = 49.15 \text{ kVAR}$$

By using the triangle, the new reactive power must be (to achieve 0.9)

$$Q_{new / phase} = 73.14 \tan(\cos^{-1}(0.9)) = 35.42 \text{ kVAR}$$

Since the motor is inductive, PF is lagging. So we need capacitors.

$$Q_{C / phase} = 35.42 - 49.15 = -13.73 \text{ kVAR}/\phi$$

