

EEEN313/ECEN405

3 Phase Power

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



1

Three phase Power

- We always are used to using single wires for all our applications. So they are called 'single phase' systems; one generator, two conductors/wires, a load.
- Now we going to do the same thing but in 'threes' –hence called three phase systems.
- For this course, we will just focus on what we call as 'balanced' three-phase systems – i.e. they are all same but just -120 and -240 degrees apart.
- Everything you know about single phase AC still relevant 😊


CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



2

So where do we start?

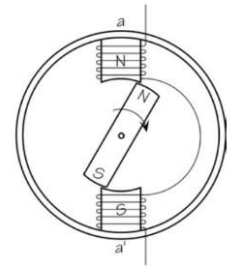- Single phase generator of course!
- Basically a magnet spinning between two pole pieces.
- So if it spins at 3000 rpm, our frequency will be 50Hz
- So what is the voltage of this? $v_a(t) = V_p \cos(\omega t)$
- Did you observe the wastage of space in the generator?
- If we put more magnets along the stator, we can get the following:



$$v_a(t) = V_p \cos(\omega t)$$

$$v_b(t) = V_p \cos(\omega t - 120^\circ)$$

$$v_c(t) = V_p \cos(\omega t - 240^\circ)$$

3 Phase Power



Three phase Systems

$$v_a(t) = V_p \cos(\omega t)$$



$$v_b(t) = V_p \cos(\omega t - 120^\circ)$$

$$v_c(t) = V_p \cos(\omega t - 240^\circ)$$

They all have the 'same' peak voltage but differ in phases by 120 degrees

This is the heart of moving almost everything in the world – from Power generation to Electric Cars and your washing machines (and all the servos in your robots and uavs)

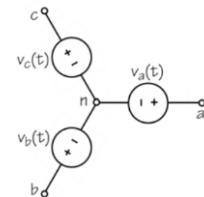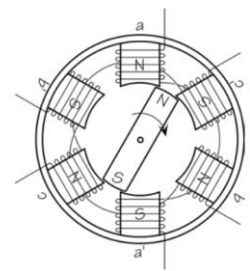As I said in the class before, if it generates power – Generator; if it consumes power – Motor




CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE

1897 VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

5

Three Phases

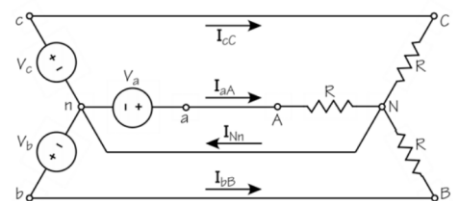- A three phase system consists of a three phase generator and a load that has three distinct sections
- The load in this sense is 'balanced' – all have same R
- There are 'four' wires – three phase wires and one neutral wire.
- Neutral wire connects to common node of the generator and the load.



$$V_a = V \angle 0^\circ$$

$$V_b = V \angle -120^\circ$$

$$V_c = V \angle -240^\circ$$

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE

1897 VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA


6

Current through the wires

$$I_{aA} = \frac{V}{R} \angle 0^\circ = \frac{V}{R} + j0$$

$$\begin{aligned} I_{bB} &= \frac{V}{R} \angle -120^\circ = \frac{V}{R} \cos(-120^\circ) + j \frac{V}{R} \sin(-120^\circ) \\ &= -0.5 \frac{V}{R} - j0.866 \frac{V}{R} \end{aligned}$$
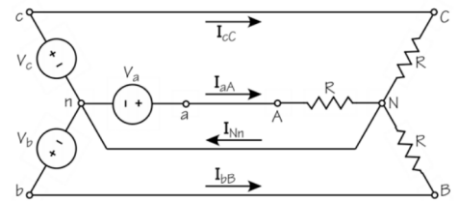
$$\begin{aligned} I_{cC} &= \frac{V}{R} \angle -240^\circ = \frac{V}{R} \cos(-240^\circ) + j \frac{V}{R} \sin(-240^\circ) \\ &= -0.5 + j0.866 \frac{V}{R} \end{aligned}$$



$$V_a = V \angle 0^\circ$$

$$V_b = V \angle -120^\circ$$

$$V_c = V \angle -240^\circ$$

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

7

Neutral Current

- At the load side, all three currents converge at the neutral node N.
- So KCL states that neutral current is sum of all the three line currents.


$$\begin{aligned} I_{Nn} &= I_{aA} + I_{bB} + I_{cC} \\ &= \frac{V}{R} - 0.5 \frac{V}{R} - j0.866 \frac{V}{R} - 0.5 + j0.866 \frac{V}{R} \\ &= 0 \end{aligned}$$

$$V_a = V \angle 0^\circ$$

$$V_b = V \angle -120^\circ$$

$$V_c = V \angle -240^\circ$$

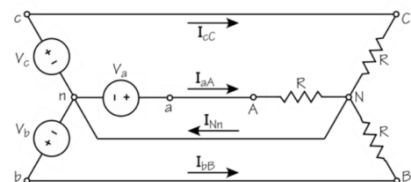- Neutral currents in a balanced system equals to zero (no neutral current).
- So if the currents all balance out to zero, so why the need for a wire?



CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE





VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

8


Conductors and Wires

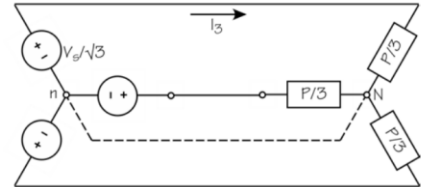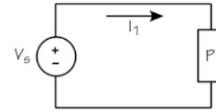- Single phase system requires two wires.
- Three phase system requires 3 wires minimum – so more power with just one extra wire.
- In reality, based on power transferred, 3 phase uses only 86.6% of metal to deliver the same power (details not included).





Other terminology

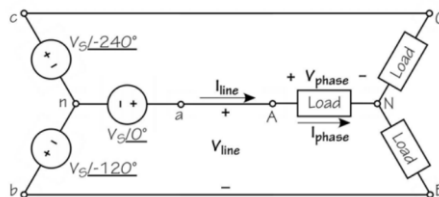- Line currents and voltages
 - Always refers to the wires of the three phase system
- Phase currents and voltages
 - Always refers to the load in the three phase system




Y and Delta connections

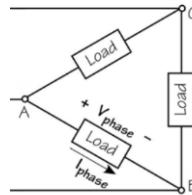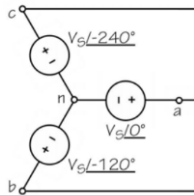

Y – Y Connection

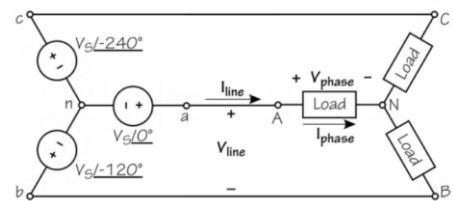- Both generation and load are connected in Y
- Line Current is current between a and A nodes
- Phase Current is through A phase of the load
- Line voltage is between two A and B phases
- Phase voltage is voltage across one phase of the load




$$I_{line} = I_{phase}$$

$$\begin{aligned} |V_{line}| &= |V_S \angle 0^\circ - V_S \angle -120^\circ| \\ &= \sqrt{3} |V_{phase}| \end{aligned}$$

Y - Δ Connection

- Generator is Y and Load is Δ

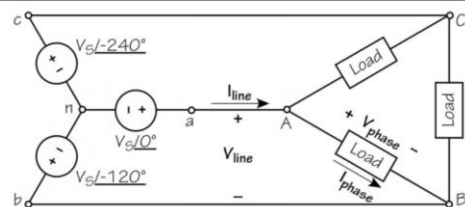

$$V_{line} = V_{phase}$$

Y connection

$$I_{line} = I_{phase}$$

$$|V_{line}| = \sqrt{3} |V_{phase}|$$

Δ connection

$$|I_{line}| = \sqrt{3} |I_{phase}|$$

$$V_{line} = V_{phase}$$

$$|I_{line}| = |I_{AB} \angle \theta - I_{CA} \angle \theta - 240^\circ|$$

$$= \sqrt{3} |I_{phase}|$$

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

13

P, Q and S – Power in 3 Phase

- If you understand the line and phase aspects of 3 phase – you know the secret handshake of the 3 phase community 😊
- For P,Q,S, lets take the Y-Y system:
- Power absorbed by a single phase in the system $P_{1\phi} = |V_{phase}| |I_{phase}| pf$
- Since all phases have same load $P_{3\phi} = 3 |V_{phase}| |I_{phase}| pf$
- For Y connected

$$P_{3\phi} = 3 \left| \frac{V_{line}}{\sqrt{3}} \right| |I_{line}| pf$$

$$= \sqrt{3} |V_{line}| |I_{line}| pf$$

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

14

P, Q and S

- For Y - Δ

- P for 3 phase will be

$$P_{3\phi} = 3|V_{line}|\left|\frac{I_{line}}{\sqrt{3}}\right|pf$$

$$= \sqrt{3}|V_{line}||I_{line}|pf$$

- So power is the same whether our system is Y connected or Δ connected provided we express our V and I in 'line' terms

- Q and S are the same too

$$P = \sqrt{3}|V_{line}||I_{line}|pf, \quad pf = \cos(\theta_v - \theta_i)$$

$$Q = \sqrt{3}|V_{line}||I_{line}|\sin(\theta_v - \theta_i)$$

$$S = \sqrt{3}V_{line}I_{line}^* = P + jQ$$

Now you are inducted into 3 Phase Society 😊

- Summary:

- Needs only 86% of the material to transport same energy
- Engineer must use line and phase to refer to connecting wires and load
- All power calculations need a $\sqrt{3}$ in their equations
- Since our restriction is to study only balanced three phase, we can reduce any system to a single phase equivalent.

Tomorrow –some examples

- So have some coffee before ☺