
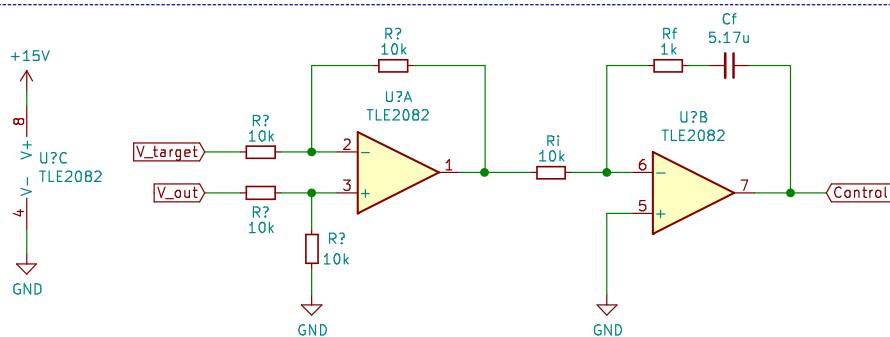


Triangle waveform generator

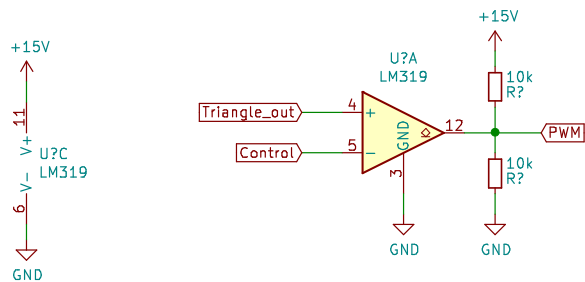


Subtraction Amplifier

PI Controller



PWM generator

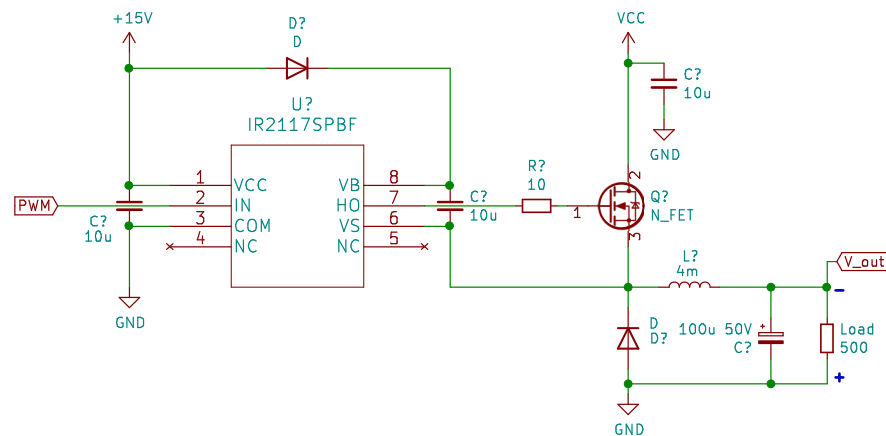

I hate this uni

Sheet: /  
File: Lab 6.sch

**Title: PI Controlled Buck Converter**

Size: User Date: 2021-09-21

KiCad E.D.A. kicad 5.1.10

**Rev: 1**

Id: 1/1