


## Characterizing the Nonlinear Loads

- Rectifiers: Nonlinear Loads
  - Power Factor (PF)
  - Displacement Power Factor (DPF)
  - Total Harmonic Distortion (THD)
- Harmonic Guideline IEEE-519

1



## Types of Rectifier Front-Ends

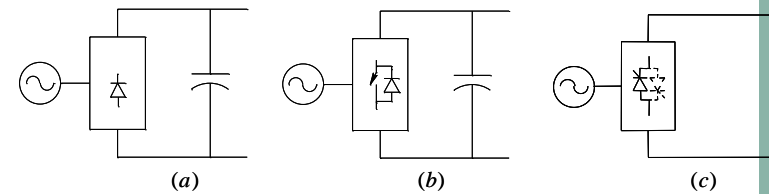


- ☐ Diode-bridge rectifiers
- ☐ Switch-mode converters
- ☐ Thyristor converter


3




### Peak-Charging Circuit

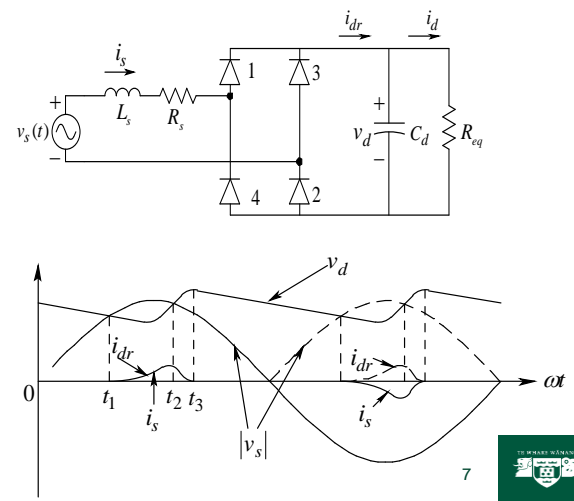

### PSpice Modeling:

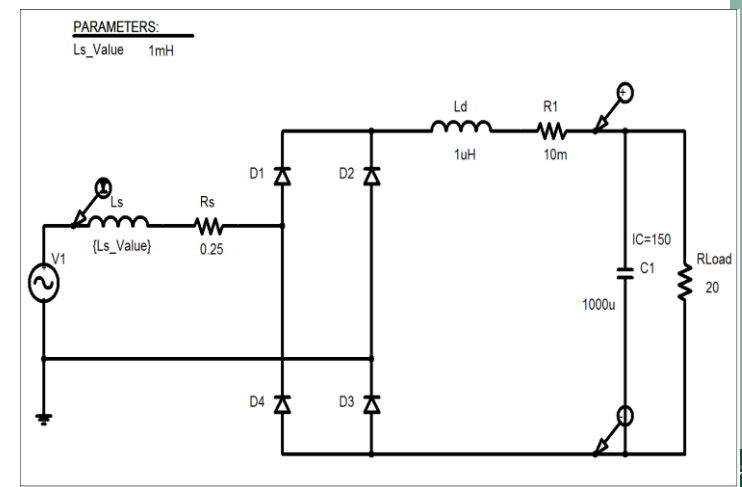



Simulation Results

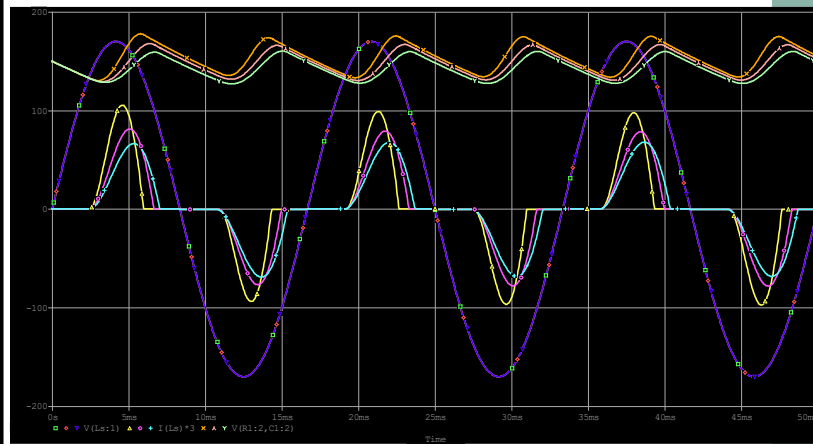

11

## Linear and Nonlinear Loads

Linear Loads

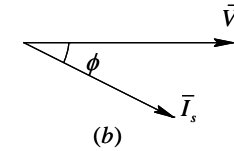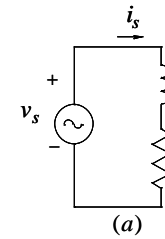


$$P = V_s I_s \cos \phi$$

$$PF = \frac{P}{V_s I_s} = \cos \phi$$

$$I_s = \frac{P}{V_s \cdot PF}$$

13

## Nonlinear Loads

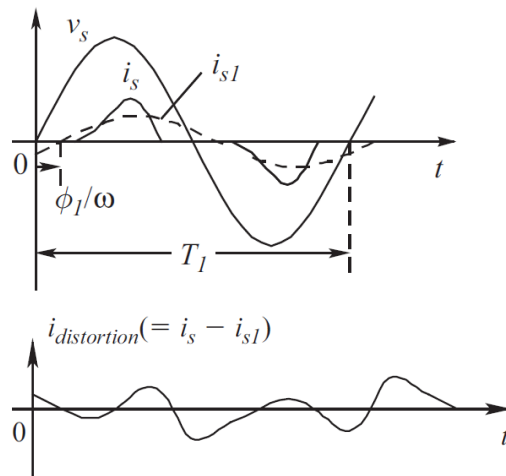

14

## Why do harmonics occur?

- When a sine wave is applied to magnetic components (Transformers, Motors, Inductors, Capacitors), The current draw from the them is nonlinear to maintain the EM.
- The magnitude of harmonic current is different for order of Harmonic.
- The lower the harmonic, the higher the current (relative)

15


## Why Harmonics

- If we have a drive that has the fundamental current of 100A at 50 Hz,
- Then current at second harmonic is 50A
- Fifth is 20A (100/5)
- 7<sup>th</sup> is 14.28
- Combining these values – 84.28
- This is the extra apparent power that the supply has to provide.
- But who uses it?

16



## Example Harmonics

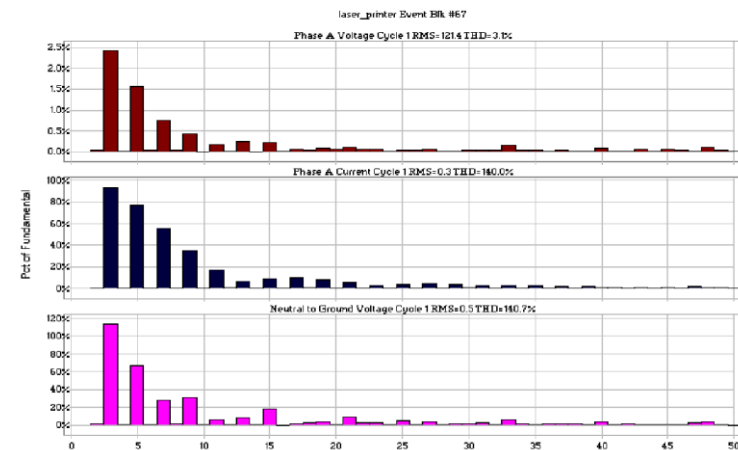

17




## Example

**Voltage:** fundamental only

**Current:** third harmonic only

**Power:** zero average

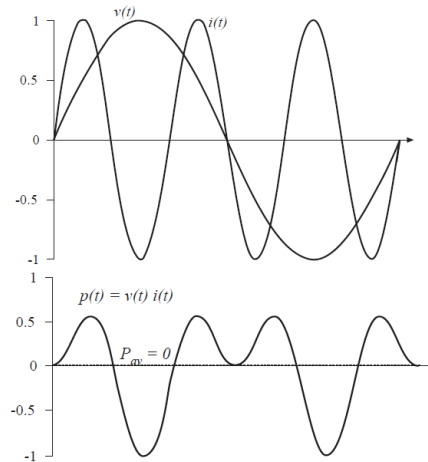

18




## Example 2

**Voltage:** third harmonic only

**Current:** third harmonic only, in phase with voltage

**Power:** nonzero average

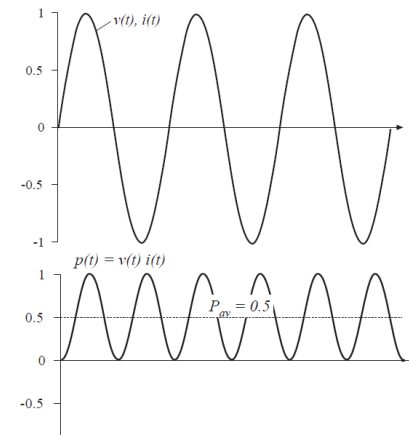

19




### Example 3

**Voltage:** 1st, 3rd, 5th

**Current:** 1st, 5th, 7th

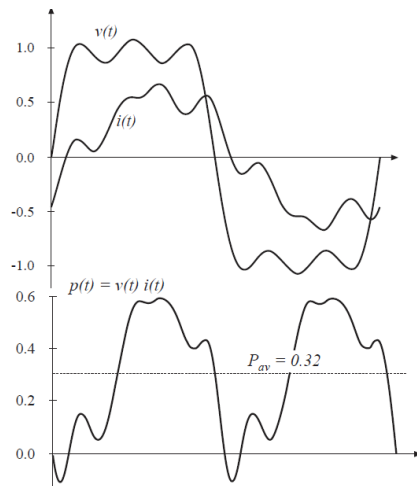
**Power:** net energy is transmitted at fundamental and fifth harmonic frequencies



20




### Current Load profiles

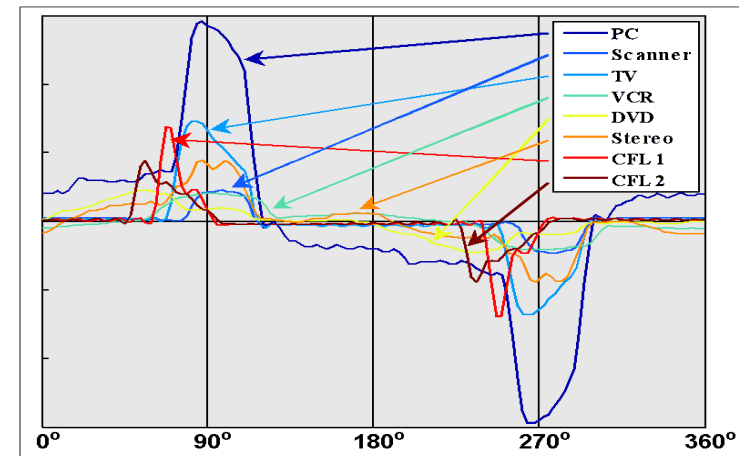

21




## Low PF

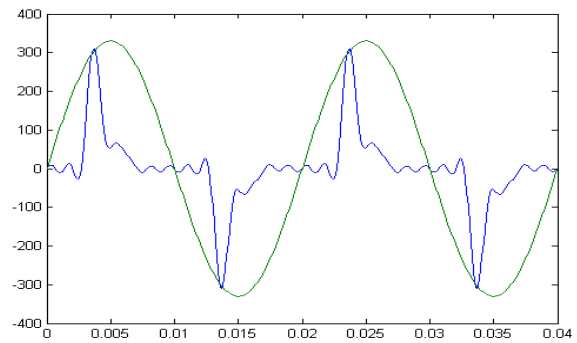

22


## High PF

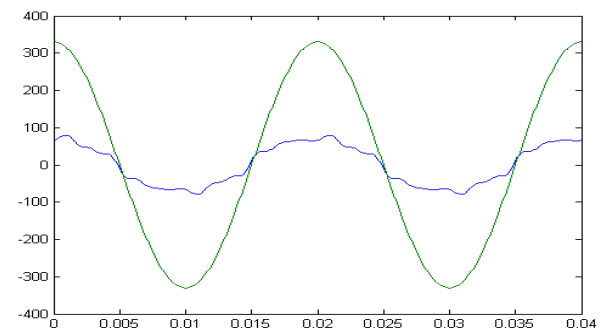

23




## LPF Harmonics

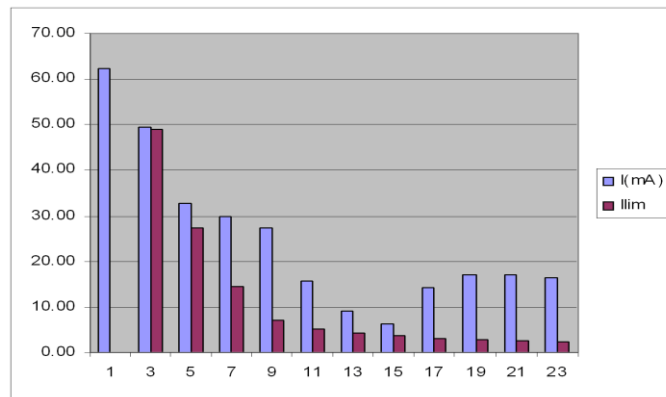

24

## HPF Harmonics

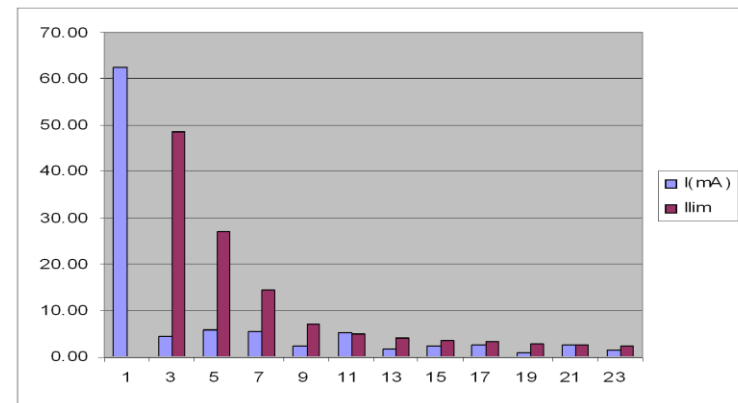

25

# Harmonic Interaction

	LPF Lamp1	LPF Lamp2	Combined Load
Power	13.5W	13.8W	27.3W
Irms	108mA	99.5mA	199mA
PF	0.51	0.56	0.57
THDi	145.25%	118.79%	128.15%
K-Factor	52.98	44.65	46.91

26




	HPF Lamp	LPF Lamp	Combined Load
Power	12.8W	13.2W	26.0W
Irms	56.4mA	99.6mA	143mA
PF	0.94	0.56	0.76
THDi	18.12%	126.85%	70.51%
K-Factor	4.83	85.60	38.66

27




## FFT of combined LPF and HPF

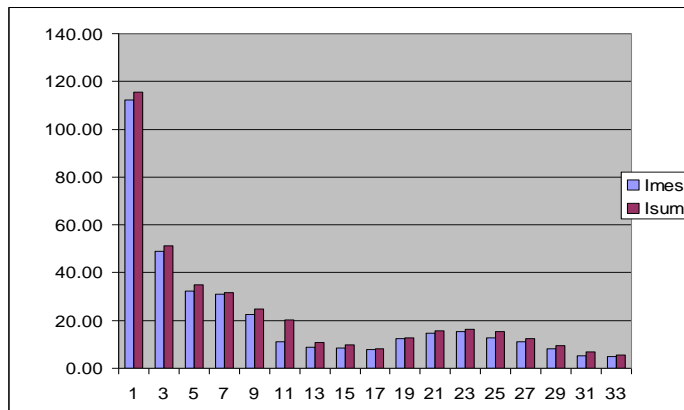

28

28

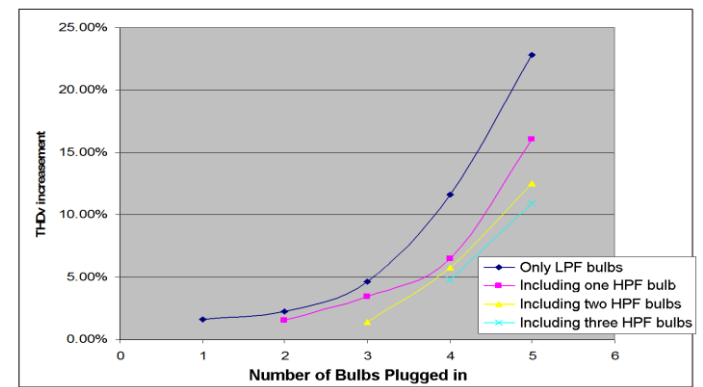

29

29

### Obtaining Harmonic Components by Fourier Analysis

$$g(t) = G_0 + \sum_{h=1}^{\infty} g_h(t) = G_0 + \sum_{h=1}^{\infty} \{a_h \cos(h\omega t) + b_h \sin(h\omega t)\}$$

$$G_0 = \frac{1}{2\pi} \int_0^{2\pi} g(t) \cdot d(\omega t)$$

$$a_h = \frac{1}{\pi} \int_0^{2\pi} g(t) \cos(h\omega t) d(\omega t) \quad h = 1, 2, \dots, \infty$$

$$b_h = \frac{1}{\pi} \int_0^{2\pi} g(t) \sin(h\omega t) d(\omega t) \quad h = 1, 2, \dots, \infty$$

$$\bar{G}_h = G_h \angle \phi_h \quad G_h = \frac{\sqrt{a_h^2 + b_h^2}}{\sqrt{2}} \quad \tan \phi_h = \frac{-b_h}{a_h}$$


$$G = \sqrt{G_0^2 + \sum_{h=1}^{\infty} G_h^2}$$

[Link](#)

30



### Nonlinear Loads

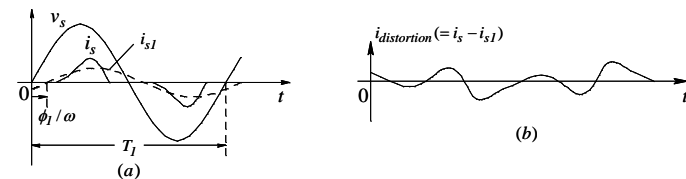

Total Harmonic Distortion:  $\%THD = 100 \times \frac{I_{distortion}}{I_{s1}}$

Displacement Power Factor:  $DPF = \cos \phi_1$

$$I_s = \sqrt{I_{s1}^2 + I_{distortion}^2}$$

$$P = V_s I_{s1} \cos \phi_1$$


$DPF$

$$PF = \frac{I_{s1}}{I_s} (DPF) = \frac{DPF}{\sqrt{1 + THD^2}}$$



31
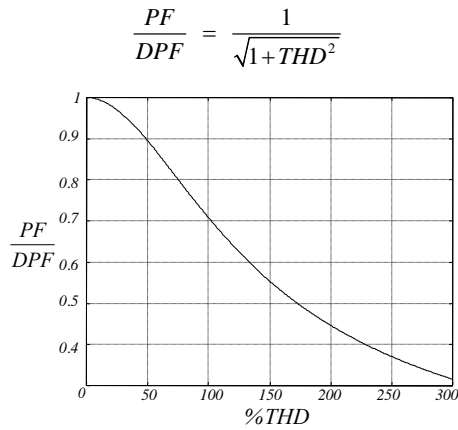
# Harmonic Currents Decrease the Power Factor -



- Ratio of actual power factor to displacement power factor decreases with increasing THD


32



# Harmonic Guidelines: IEEE – 519

$I_{SC} / I_1$	Odd Harmonic Order $h$					Total Harmonic Distortion(%)
	$h < 11$	$11 \leq h \leq 17$	$17 \leq h \leq 23$	$23 \leq h \leq 35$	$35 \leq h$	
$< 20$	4.0	2.0	1.5	0.6	0.3	5.0
20 – 50	7.0	3.5	2.5	1.0	0.5	8.0
50 – 100	10.0	4.5	4.0	1.5	0.7	12.0
100 – 1000	12.0	5.5	5.0	2.0	1.0	15.0
$> 1000$	15.0	7.0	6.0	2.5	1.4	20.0

Short-Circuit Current:  $I_{SC}$

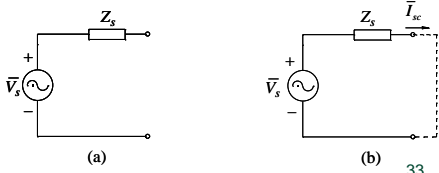

33



## Harmonic Guidelines: IEEE - 519

$I_{SC} / I_L$	Odd Harmonic Order $h$					Total Harmonic Distortion(%)
	$h < 11$	$11 \leq h \leq 17$	$17 \leq h \leq 23$	$23 \leq h \leq 35$	$35 \leq h$	
$< 20$	4.0	2.0	1.5	0.6	0.3	5.0
20 – 50	7.0	3.5	2.5	1.0	0.5	8.0
50 – 100	10.0	4.5	4.0	1.5	0.7	12.0
100 – 1000	12.0	5.5	5.0	2.0	1.0	15.0
$> 1000$	15.0	7.0	6.0	2.5	1.4	20.0

- ☐ Limits on allowable harmonic currents drawn by loads of various relative magnitudes
- ☐ Relative magnitude of load currents is based on Short Circuit Ratio (SCR)

34



## AS/NZS 61000.3.2 (2009)

**Table 3 – Limits mainly for Class D equipment**

NOTE - Refer to Clause 7.3b) for limits for Class C equipment

Harmonic order $n$	Maximum permissible harmonic current per watt mA/W	Maximum permissible harmonic current A
3	3,4	2,30
5	1,9	1,14
7	1,0	0,77
9	0,5	0,40
11	0,35	0,33
$13 \leq n \leq 39$ (odd harmonics only)	$\frac{3,85}{n}$	See Table 1

35



## Summary

### Characterizing the Nonlinear Loads

- Diode Rectifiers as Nonlinear Loads
  - Power Factor (PF)
  - Displacement Power Factor (DPF)
  - Total Harmonic Distortion (THD)
- Harmonic Guideline IEEE-519

36



## Concept Quiz

For a given Power  $P$  drawn by a load at a given voltage level, the current drawn by that load is larger in magnitude if the power factor is smaller.

- A. True (**correct**)
- B. False

37



## Clicker Quiz

A power-electronic load is supplied by a sinusoidal utility-source with the rms voltage of 120 V. The rms value of the current drawn is 10 A. The fundamental-frequency component of the current drawn has the rms value of 8 A, and it lags the utility voltage waveform by 15 degrees.

Calculate the power factor of operation for this load.

- A. 0.966
- B. 0.773
- C. 0.8
- D. None of the above

38

