

ECEN405 Lab 5 Report

Buck-Boost Converter


Niels Clayton : 300437590
Lab Partner: Daniel Eisen

1 Design

$V_d = 10V, R_L = 500\Omega, L = 4mH, C = 100\mu F, D = 0.6, D_{max} = 0.67$


Switching Frequency
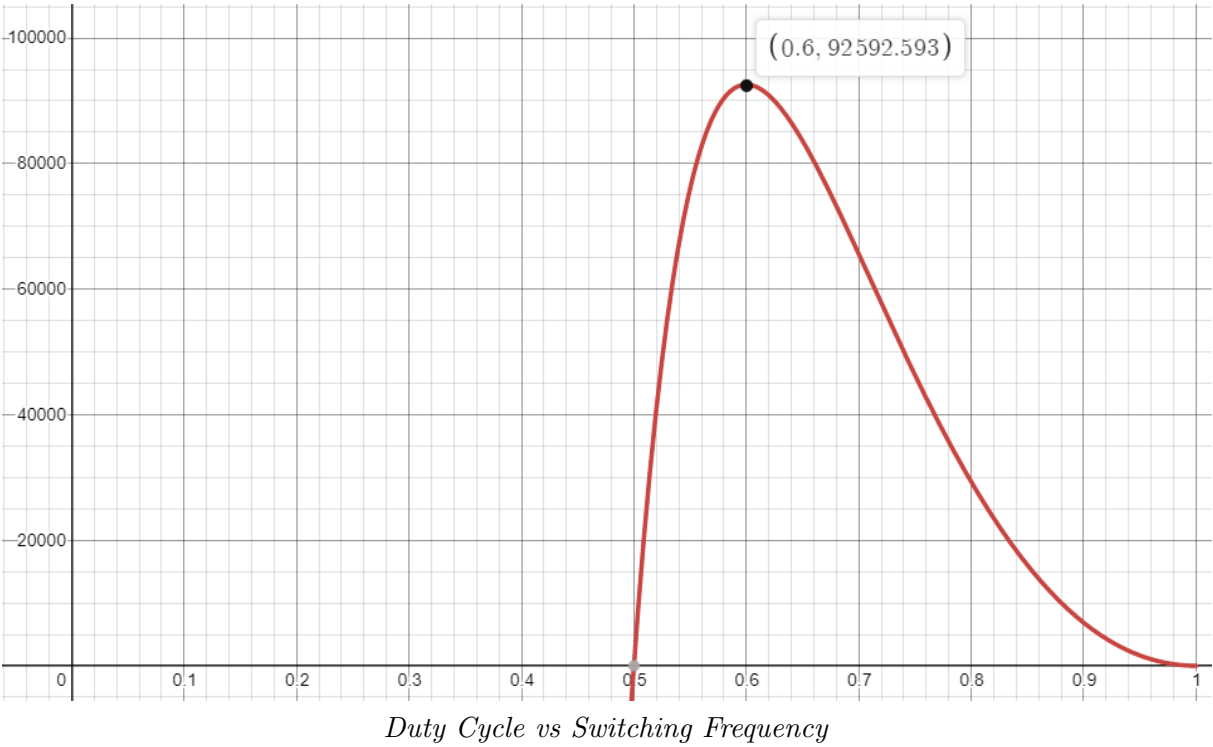
$$V_o = \frac{D}{1-D}V_d = 15V$$
$$I_o = \frac{V_o}{R_L} = 0.03A$$
$$I_{ripple} = 0.2I_o\frac{V_o}{V_d} = 0.009A$$
$$I_{omax} = I_o + 0.5I_{ripple} = 0.0345A$$
$$f_{sw} = \frac{V_d(V_o - V_d)}{LI_{ripple}V_o} = 92592.5925926Hz$$



Note that a 60% duty cycle requires the highest switching frequency.

Schematic

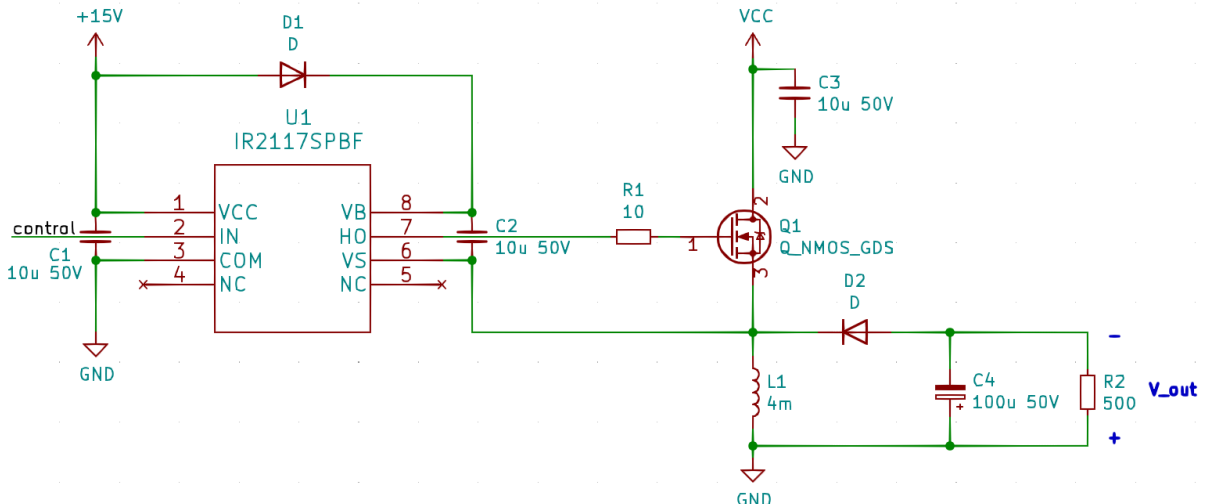

Output Voltage Ripple


$$V_{ripple} = \frac{I_{omax}D_{max}}{f_{sw}C} = 0.00425V$$

2 Output

The USB drive with the "real" screenshots are still in the lab plugged into the computer with a half written report on it.

In light of this misplacement we have acquired an artistic recreation of the signal, based on first person accounts of the original waveform.

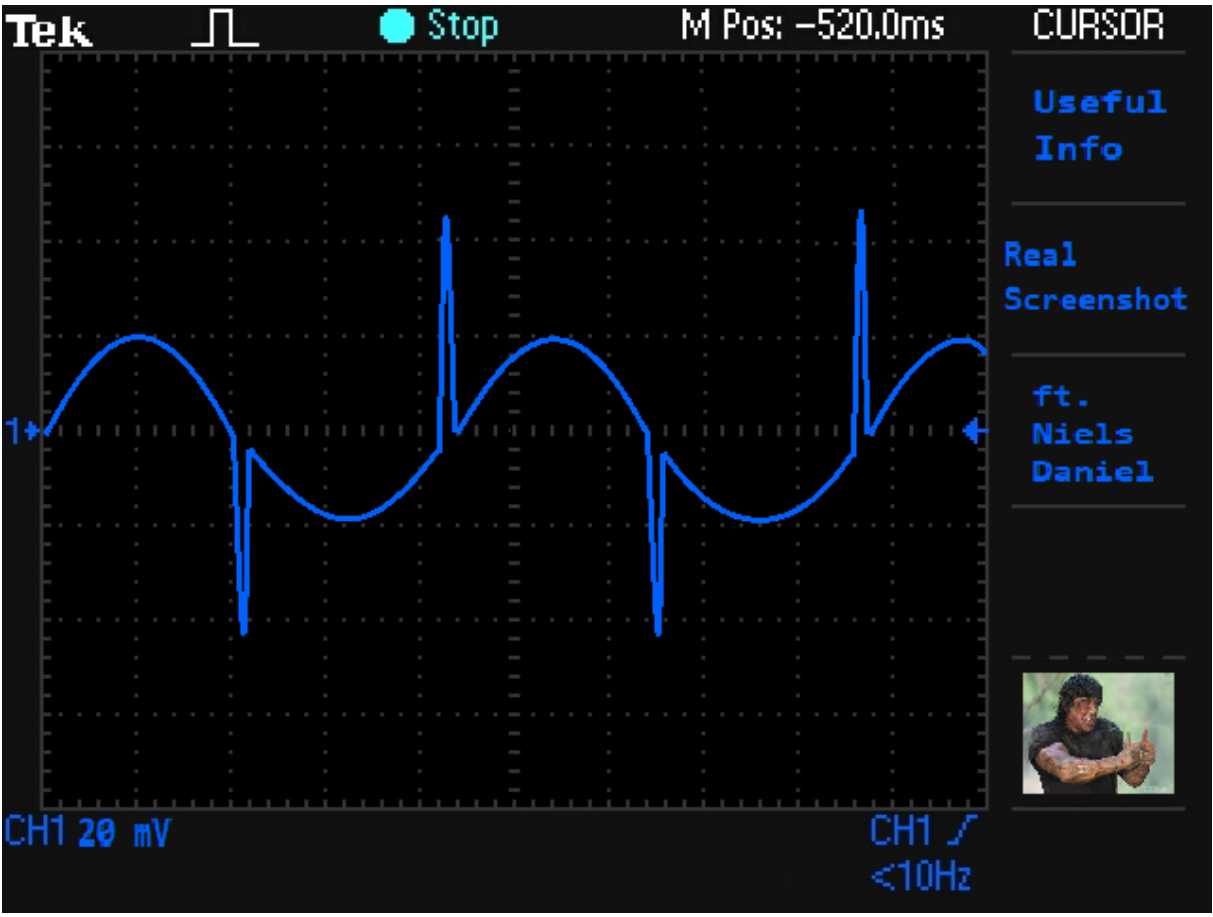As shown from the image below, it can be remembered that there was a substantial output voltage ripple, with possible peaks of 20 mV, and large transients at the locations of the switching.



3 Efficiency

