

EEEN313/ECEN405

Power Calculations 2

Engineering Quotes:

"A good engineer is someone who can do for a dime what any darn fool can do for a dollar."


CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



1


Inductors and Capacitors

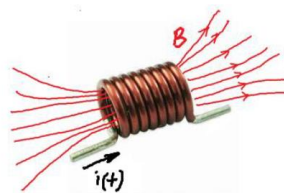- **Ideal** inductors and capacitors are solely energy storage circuit elements
- On average they do not dissipate power
- They simply absorb (store) energy and subsequently release it



Inductors store energy in magnetic field

$$w(t) = \frac{1}{2} Li^2(t)$$

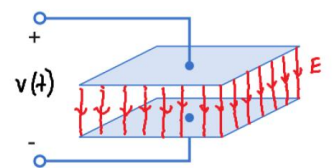

Capacitors store energy in electric field

$$w(t) = \frac{1}{2} Cv^2(t)$$


CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



2


Inductor Average Power

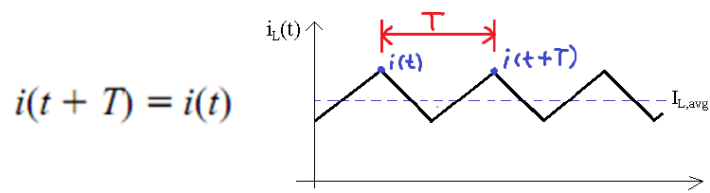- If the inductor is periodic, the stored energy at the end of one period is same as at the beginning



3

V, I, P for an Inductor

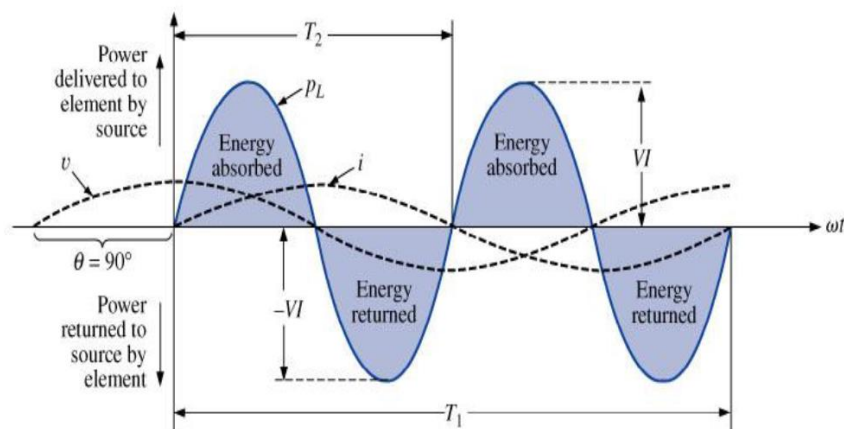

5

Inductor Average Voltage

- From the V-I relationship for an inductor

$$i(t_0 + T) = \frac{1}{L} \int_{t_0}^{t_0+T} v_L(t) dt + i(t_0)$$

- As starting and ending values are same for periodic currents


$$i(t_0 + T) - i(t_0) = \frac{1}{L} \int_{t_0}^{t_0+T} v_L(t) dt = 0$$

$$\text{avg}[v_L(t)] = V_L = \frac{1}{T} \int_{t_0}^{t_0+T} v_L(t) dt = 0$$

This is very important conclusion which is used in the analysis of switching converters


Same for Capacitor

$$v(t + T) = v(t)$$

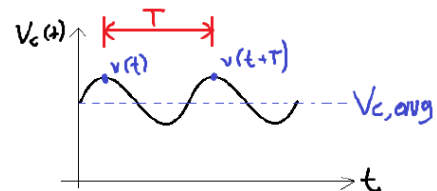

$$P_{c,avg} = \frac{1}{2} C \underbrace{[v(t+T)^2 - v(t)^2]}_0 = 0$$

V, I, P of Capacitor

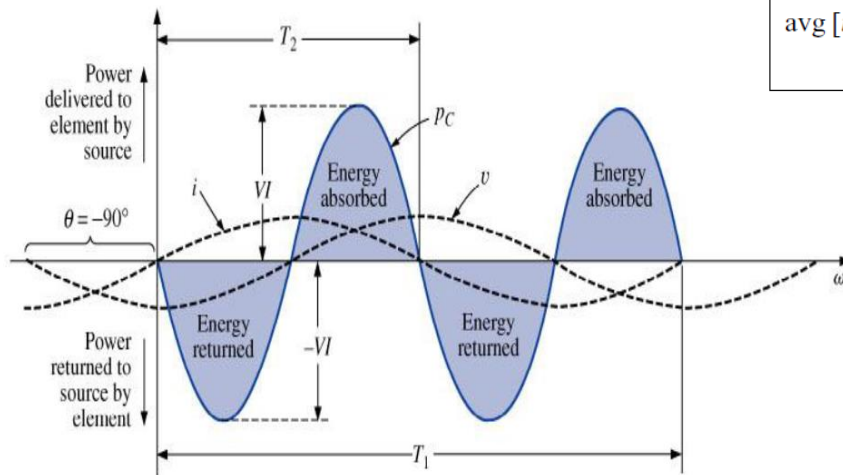

$$\text{avg}[i_C(t)] = I_C = \frac{1}{T} \int_{t_0}^{t_0+T} i_C(t) dt = 0$$


This is very important conclusion which is used in the analysis of switching converters

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE

1837 VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

8

Border of CCM and DCM of an Inductor

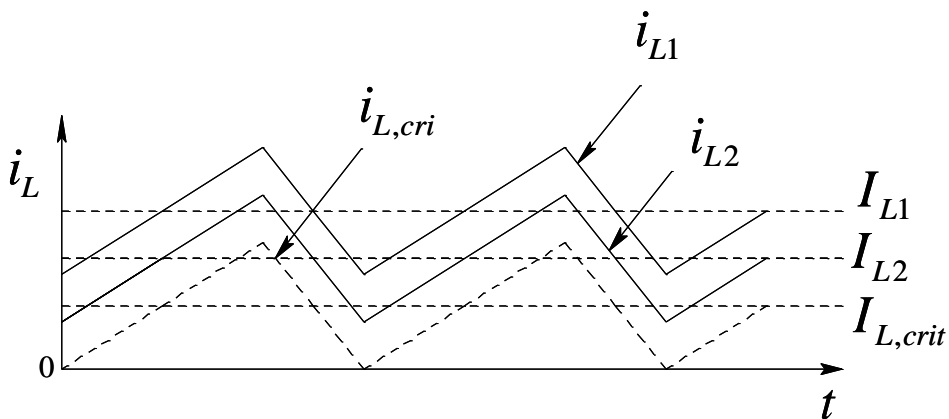

CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE


1837 VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

9

Energy Recovery

- For periodic operations, net energy in L and C must be zero in steady state condition, otherwise, leading to voltage and current ramp-ups
- Circuit efficiency can be improved if energy can be transferred **to the load (or supply)** rather than dissipated in circuit

Energy Recovery

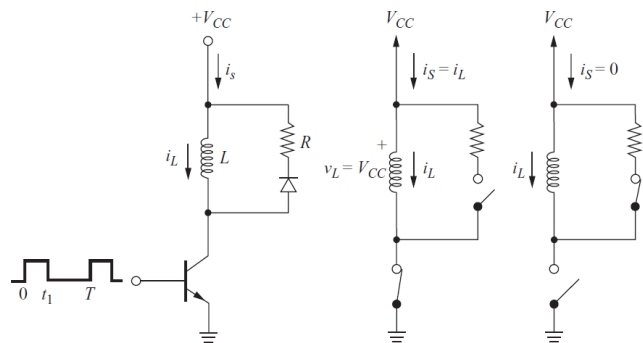


$$i_L(t) = \frac{1}{L} \int_0^t v_L(t) dt + i_L(0) = \frac{1}{L} \int_0^t V_{CC} dt + 0 = \frac{V_{CC}t}{L}$$

$$i_L(t) = \left(\frac{V_{CC}t_1}{L} \right) e^{-(t-t_1)/\tau}$$

Energy Recovery - NOT

$$i_L(t) = \left(\frac{V_{CC} t_1}{L} \right) e^{-(t-t_1)/\tau}$$
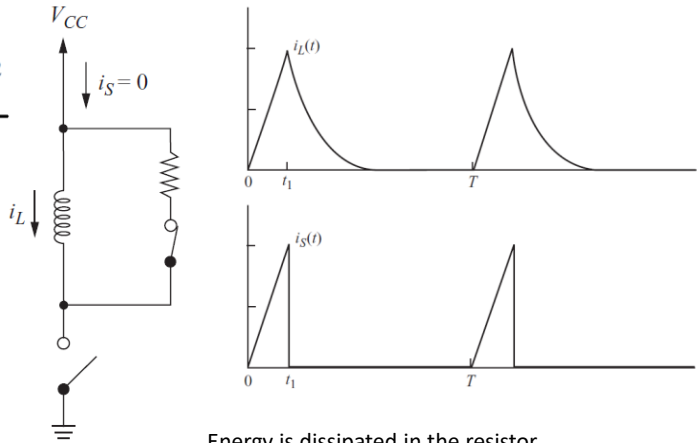
$$P_R = P_s = \frac{(V_{CC} t_1)^2}{2LT}$$



Energy is dissipated in the resistor


CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

15

Energy Recovery

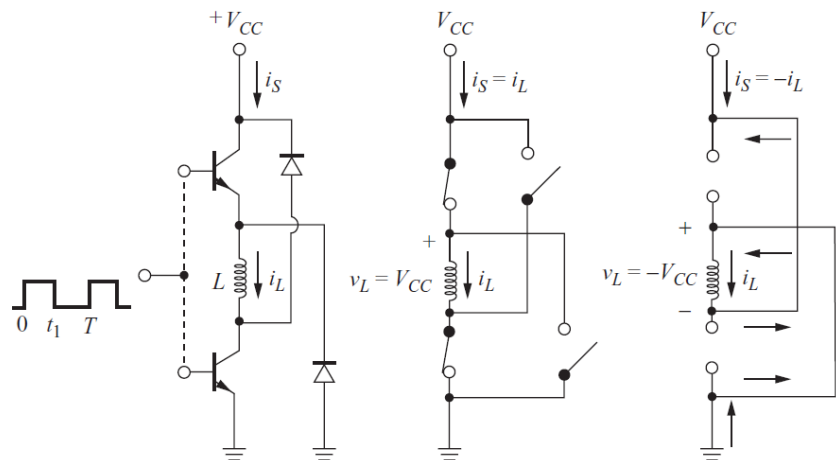


CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA


16

Energy Recovery

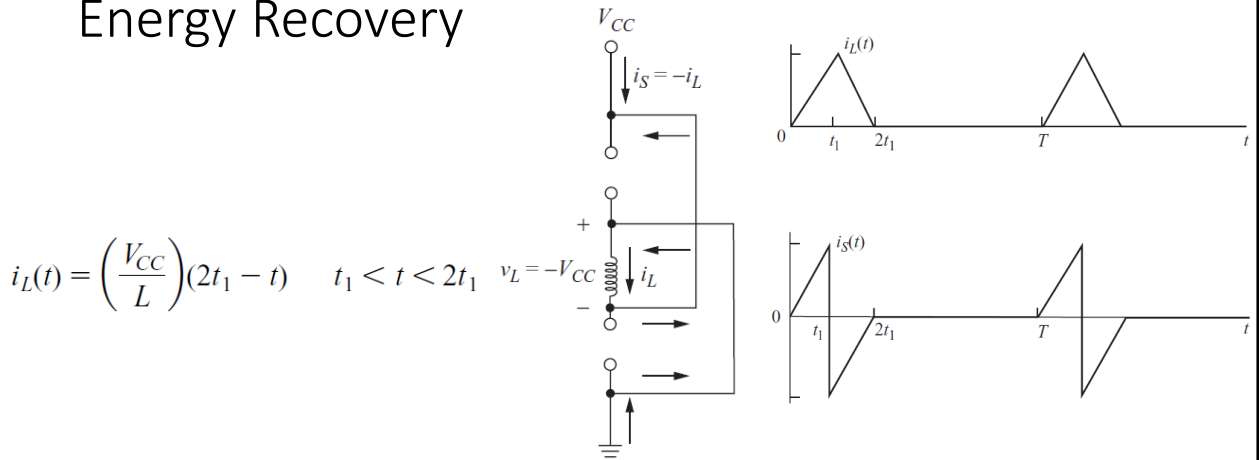


Sinusoidal AC Circuits

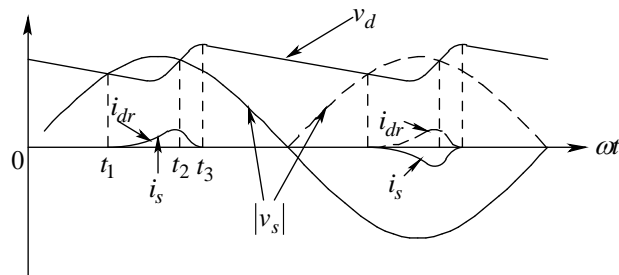- Voltages and Currents in PE converters are non-sinusoidal
- A non-sinusoidal periodic waveform can be represented by a Fourier series of sinusoids



Current Waveform Examples

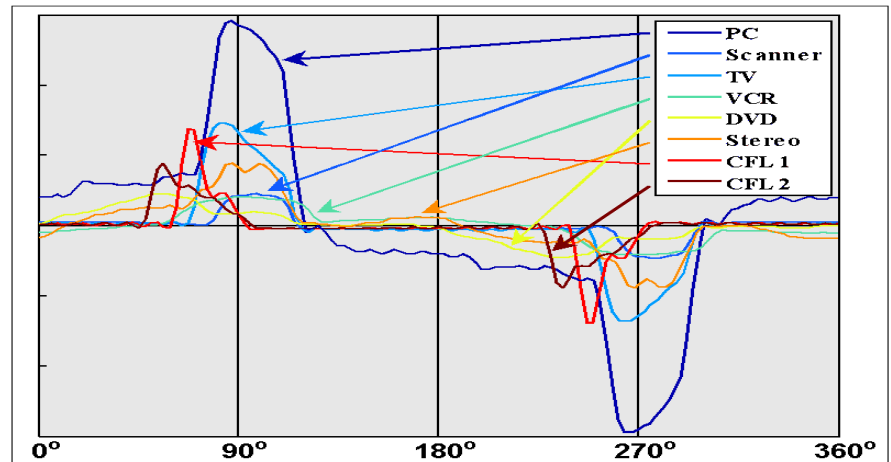

Average Power Calculations

- If periodic voltage and current waveforms represented by the Fourier series as
- Then the average power is computed as

$$v(t) = V_0 + \sum_{n=1}^{\infty} V_n \cos(n\omega_0 t + \theta_n)$$

$$i(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos(n\omega_0 t + \phi_n)$$

$$P = \frac{1}{T} \int_0^T v(t)i(t) dt$$

$$P = \sum_{n=0}^{\infty} P_n = V_0 I_0 + \sum_{n=1}^{\infty} V_{n,\text{rms}} I_{n,\text{rms}} \cos(\theta_n - \phi_n)$$


- Note that total average power is the sum of the powers at the frequencies in the Fourier series

$$P = V_0 I_0 + \sum_{n=1}^{\infty} \left(\frac{V_{n,\text{max}} I_{n,\text{max}}}{2} \right) \cos(\theta_n - \phi_n)$$

Non-sinusoidal Source – Linear Load

- If a non-sinusoidal periodic voltage is applied to a linear load the power absorbed by the load can be determined by using superposition
- A non-sinusoidal periodic voltage is equivalent to the series combination of the Fourier series voltages

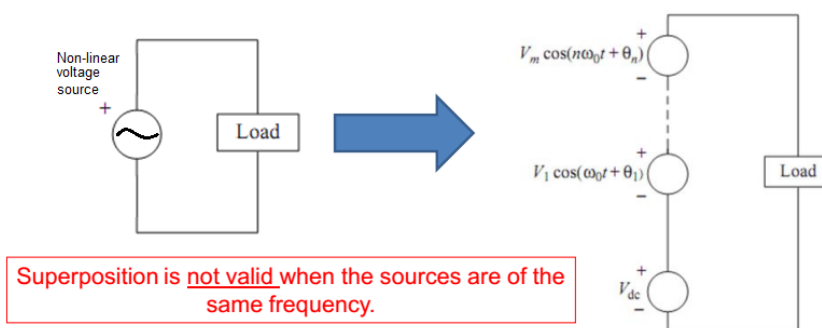- The current in the load can be determined using superposition




Example

- A non-sinusoidal voltage source has a fourier series of

$$v(t) = 10 + 20 \cos(2\pi 60t - 25^\circ) + 30 \cos(4\pi 60t + 20^\circ) \text{ V}$$

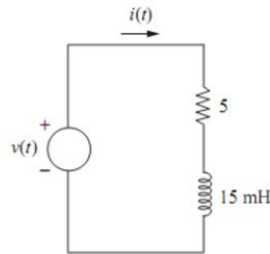- This voltage is connected to a load that is 5 ohm resistor and 15 mH inductor in series.
- Determine the power absorbed by the load.



Solution

- The dc term is

$$I_0 = \frac{V_0}{R} = \frac{10}{5} = 2 \text{ A}$$


- AC current terms are computed from phasor analysis:

$$I_1 = \frac{V_1}{R + j\omega_1 L} = \frac{20 \angle (-25^\circ)}{5 + j(2\pi 60)(0.015)} = 2.65 \angle (-73.5^\circ) \text{ A}$$

$$I_2 = \frac{V_2}{R + j\omega_2 L} = \frac{30 \angle 20^\circ}{5 + j(4\pi 60)(0.015)} = 2.43 \angle (-46.2^\circ) \text{ A}$$

- Load current then can be calculated as
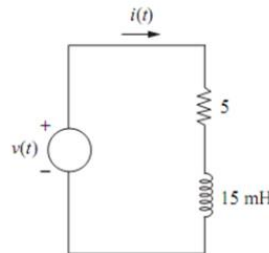
$$i(t) = 2 + 2.65 \cos(2\pi 60t - 73.5^\circ) + 2.43 \cos(4\pi 60t - 46.2^\circ) \text{ A}$$



Power Absorbed

- The power at each frequency in the Fourier series can be determined as follows,

dc term: $P_0 = (10 \text{ V})(2 \text{ A}) = 20 \text{ W}$

$\omega = 2\pi 60$: $P_1 = \frac{(20)(2.65)}{2} \cos(-25^\circ + 73.5^\circ) = 17.4 \text{ W}$


$\omega = 4\pi 60$: $P_2 = \frac{(30)(2.43)}{2} \cos(20^\circ + 46^\circ) = 14.8 \text{ W}$

- Total power is then

$$P = 20 + 17.4 + 14.8 = 52.2 \text{ W}$$

- Alternative Method:** Since the average power of inductor is zero, the power absorbed by the load can be calculated using rms current as follows
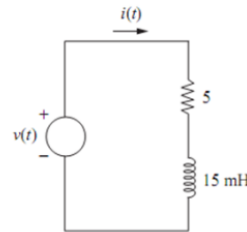
$$P = I_{\text{rms}}^2 R = \left[2^2 + \left(\frac{2.65}{\sqrt{2}} \right)^2 + \left(\frac{2.43}{\sqrt{2}} \right)^2 \right] 5 = 52.2 \text{ W}$$




Sinusoidal Source and Nonlinear Load

- If a sinusoidal voltage source is applied to a nonlinear load, the current waveform will not be sinusoidal but can be represented as a Fourier series
- Voltage source is linear

$$v(t) = V_1 \sin(\omega_0 t + \theta_1)$$

- Current is represented by Fourier
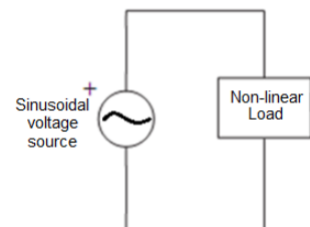
$$i(t) = I_0 + \sum_{n=1}^{\infty} I_n \sin(n\omega_0 t + \phi_n)$$



- Average power absorbed by the load is computed as

$$\begin{aligned}
 P &= V_0 I_0 + \sum_{n=1}^{\infty} \left(\frac{V_{n,\max} I_{n,\max}}{2} \right) \cos(\theta_n - \phi_n) \\
 &= (0)(I_0) + \left(\frac{V_1 I_1}{2} \right) \cos(\theta_1 - \phi_1) + \sum_{n=2}^{\infty} \frac{(0)(I_{n,\max})}{2} \cos(\theta_n - \phi_n) \\
 &= \left(\frac{V_1 I_1}{2} \right) \cos(\theta_1 - \phi_1) = V_{1,\text{rms}} I_{1,\text{rms}} \cos(\theta_1 - \phi_1)
 \end{aligned}$$

Note that the only nonzero power term is at the frequency of the applied voltage!!!

- Power factor of the load

$$\text{pf} = \frac{P}{S} = \frac{P}{V_{\text{rms}} I_{\text{rms}}}$$

$$\text{pf} = \frac{V_{1,\text{rms}} I_{1,\text{rms}} \cos(\theta_1 - \phi_1)}{V_{1,\text{rms}} I_{\text{rms}}} = \left(\frac{I_{1,\text{rms}}}{I_{\text{rms}}} \right) \cos(\theta_1 - \phi_1)$$

- RMS current is computed

$$I_{\text{rms}} = \sqrt{\sum_{n=0}^{\infty} I_{n,\text{rms}}^2} = \sqrt{I_0^2 + \sum_{n=1}^{\infty} \left(\frac{I_n}{\sqrt{2}} \right)^2}$$

Power Indices

- Note that the power factor term commonly used in linear circuits is called the **displacement power factor**

$$\text{pf} = \cos(\theta_1 - \phi_1)$$

- The **distortion factor** (DF) describes the reduction in power factor as a result of the nonlinear distortion, and from the PF expression for distorted voltage:

$$\text{DF} = \frac{I_{1, \text{rms}}}{I_{\text{rms}}} \quad \text{pf} = [\cos(\theta_1 - \phi_1)] \text{DF}$$

THD

- THD is the ratio of the rms value of all the non-fundamental frequency terms to the rms value of the fundamental frequency term

• or

$$\text{THD} = \sqrt{\frac{\sum_{n \neq 1} I_{n, \text{rms}}^2}{I_{1, \text{rms}}^2}} = \frac{\sqrt{\sum_{n \neq 1} I_{n, \text{rms}}^2}}{I_{1, \text{rms}}}$$

$$\text{THD} = \sqrt{\frac{I_{\text{rms}}^2 - I_{1, \text{rms}}^2}{I_{1, \text{rms}}^2}} \quad \text{DF} = \sqrt{\frac{1}{1 + (\text{THD})^2}}$$

Apparent Power

- Since only non-zero term for reactive power is at the frequency of voltage, the reactive power can be expressed as

$$Q = \frac{V_1 I_1}{2} \sin(\theta_1 - \phi_1)$$

- With P and Q defined for the non-sinusoidal case, apparent power S must include a term to account for the current at frequencies which are different from the voltage frequency

S

- The term **distortion volt-amps D** is traditionally used in the computation of S

$$S = \sqrt{P^2 + Q^2 + D^2}$$



$$D = V_{1, \text{rms}} \sqrt{\sum_{n \neq 1}^{\infty} I_{n, \text{rms}}^2} = \frac{V_1}{2} \sqrt{\sum_{n \neq 1}^{\infty} I_n^2}$$

Factors

- Other terms that are sometimes used for non-sinusoidal current (or voltages) are **form factor** and **crest factor**

$$\text{Form factor} = \frac{I_{\text{rms}}}{I_{\text{avg}}}$$
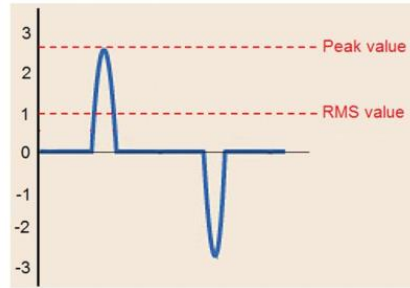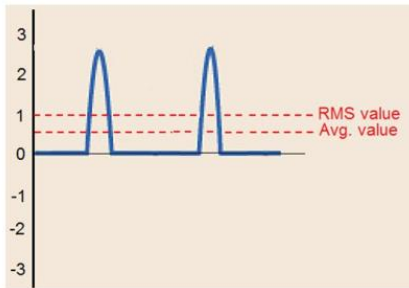
$$\text{Crest factor} = \frac{I_{\text{peak}}}{I_{\text{rms}}}$$



CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA


37

Example

- A sinusoidal voltage source of $v(t) = 100 \cos(377t)$ V is applied to a nonlinear load, resulting in a non-sinusoidal current which is expressed in Fourier series form as

$$i(t) = 8 + 15 \cos(377t + 30^\circ) + 6 \cos[2(377)t + 45^\circ] + 2 \cos[3(377)t + 60^\circ]$$

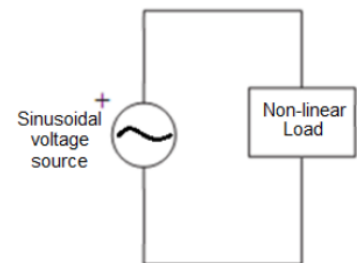- Determine,
 - The power absorbed by the load
 - The power factor of the load
 - The distortion factor of the load current
 - The total harmonic distortion of the load current



CAPITAL THINKING.
GLOBALLY MINDED.
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA

38

Solution

- a) The power absorbed by the load is determined by computing the power absorbed at each frequency in the Fourier series

$$P = (0)(8) + \left(\frac{100}{\sqrt{2}}\right)\left(\frac{15}{\sqrt{2}}\right)\cos 30^\circ + (0)\left(\frac{6}{\sqrt{2}}\right)\cos 45^\circ + (0)\left(\frac{2}{\sqrt{2}}\right)\cos 60^\circ$$

$$P = \left(\frac{100}{\sqrt{2}}\right)\left(\frac{15}{\sqrt{2}}\right)\cos 30^\circ = 650 \text{ W}$$

- b) The rms voltage and rms current are

$$V_{\text{rms}} = \frac{100}{\sqrt{2}} = 70.7 \text{ V} \quad I_{\text{rms}} = \sqrt{8^2 + \left(\frac{15}{\sqrt{2}}\right)^2 + \left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{2}{\sqrt{2}}\right)^2} = 14.0 \text{ A}$$

then the power factor is

$$\text{pf} = \frac{P}{S} = \frac{P}{V_{\text{rms}} I_{\text{rms}}} = \frac{650}{(70.7)(14.0)} = 0.66$$

Solution

- c) The distortion factor is computed as

$$\text{DF} = \frac{I_{1,\text{rms}}}{I_{\text{rms}}} = \frac{\frac{15}{\sqrt{2}}}{14.0} = 0.76$$

- d) The total harmonic distortion of the load current is obtained as

$$\text{THD} = \sqrt{\frac{I_{\text{rms}}^2 - I_{1,\text{rms}}^2}{I_{1,\text{rms}}^2}} = \sqrt{\frac{14^2 - \left(\frac{15}{\sqrt{2}}\right)^2}{\left(\frac{15}{\sqrt{2}}\right)^2}} = 0.86 = 86\%.$$

**CAPITAL THINKING.
GLOBALLY MINDED.**
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF
WELLINGTON
TE HERENGA WAKA