

ECEN405 Lab 6 Report

Niels Clayton : 300437590

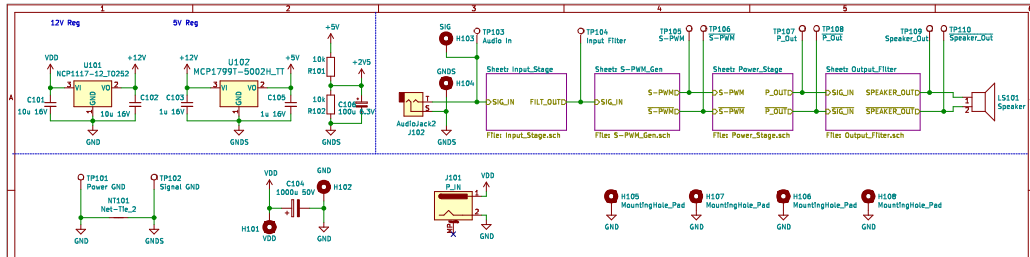


Figure 1: High level design schematic

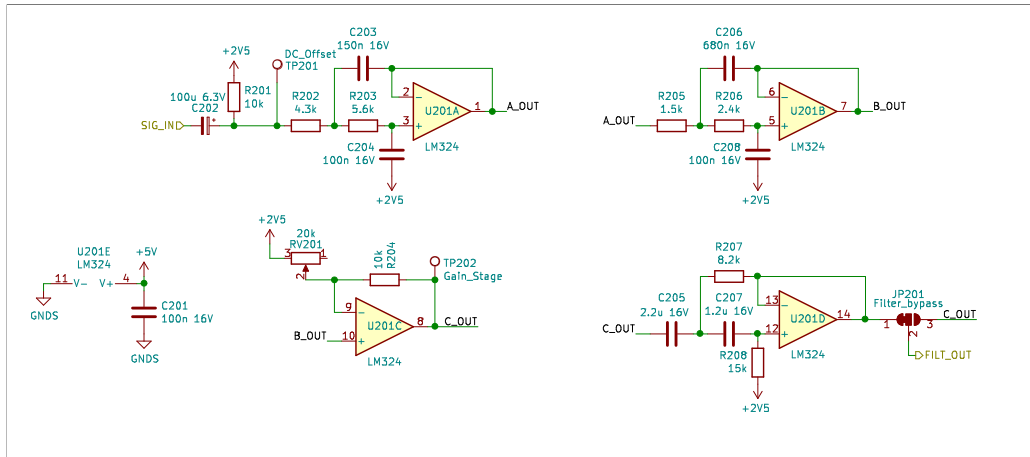


Figure 2: Input filtering schematic

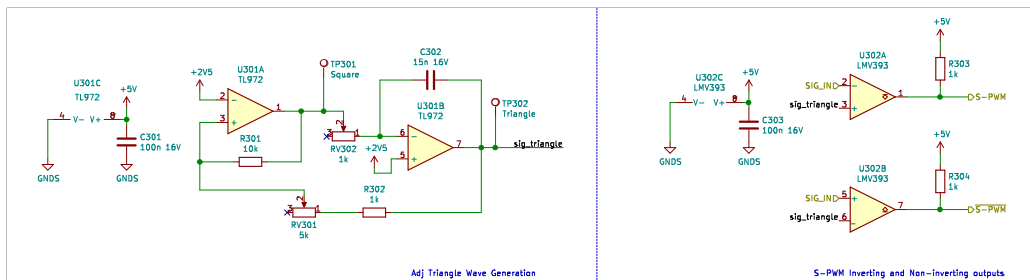


Figure 3: Sampling triangle wave & SPWM generation schematic

 


Figure 4: Gate driver schematic

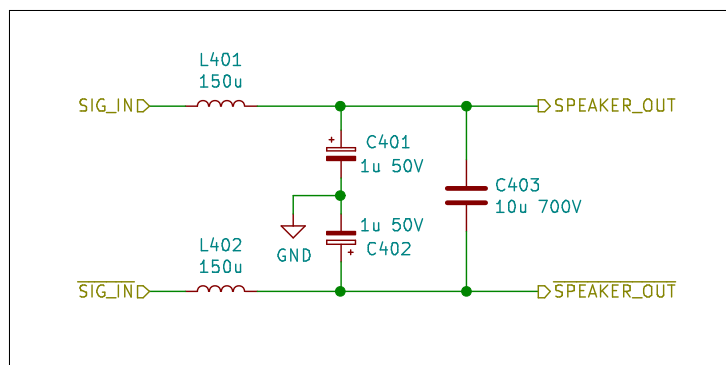


Figure 5: Output filter schematic