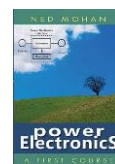


# EEEN313/ECEN405

## Converters for Electric Drives

Reading: Chapter 11: Ned Mohan – Power Electronics A first Course




CAPITAL THINKING.  
GLOBALLY MINDED.  
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF  
**WELLINGTON**  
TE HERENGA WAKA

1

### Adjustable-Speed Drive:

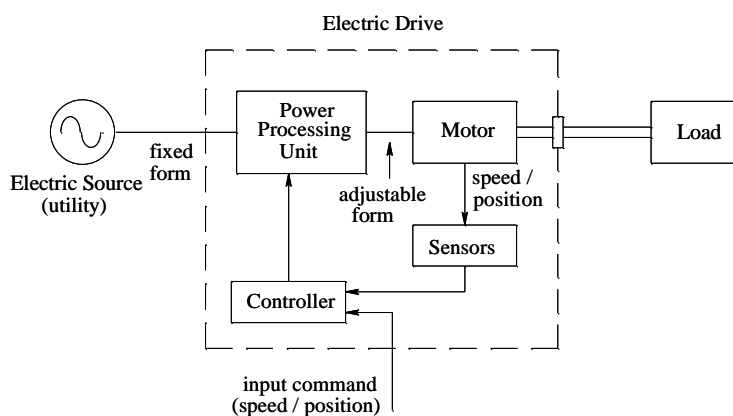


CAPITAL THINKING.  
GLOBALLY MINDED.  
MAI I TE IHO KI TE PAE



VICTORIA UNIVERSITY OF  
**WELLINGTON**  
TE HERENGA WAKA

2

DC MOTORS

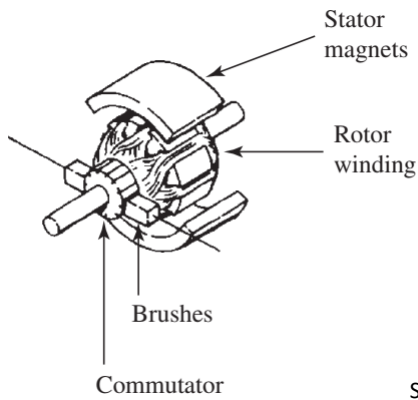


Source: Electro-Craft Corporation.

DC-Machine Equivalent Circuit

$$v_a = e_a + R_a i_a + L_a \frac{di_a}{dt}$$
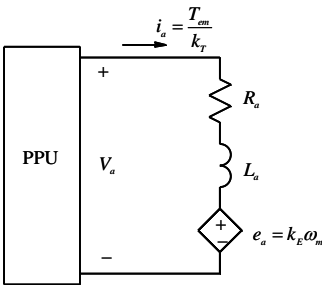
$$\frac{d\omega_m}{dt} = \frac{1}{J_{eq}} (T_{em} - T_L)$$





$$k_T = k_E$$


Torque-Speed Characteristics

$$V_a = k_E \omega_m + R_a I_a$$

$$I_a = \frac{T_{em} (= T_L)}{k_T}$$

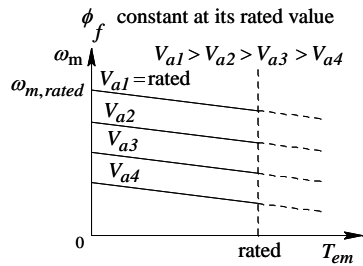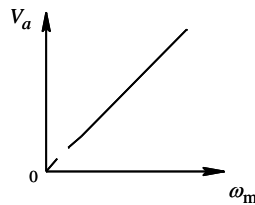

PERMANENT-MAGNET AC MACHINES

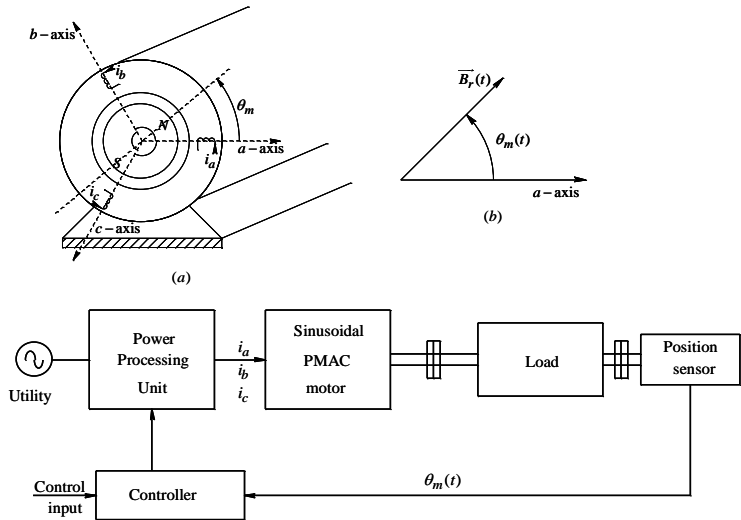

In ac steady state, accounting all three-phases, the input electric power, supplied by the current in opposition to the induced back-emf, equals the mechanical output power

$$T_{em} \omega_m = 3 \underbrace{(k_{E,phase} \omega_m)}_{E_{rms}} I_{rms}$$

The torque contribution of each phase is  $T_{em}/3$ ,

$$T_{em,phase} = \frac{T_{em}}{3} = k_{E,phase} I_{rms}$$

The electromagnetic torque acts on the mechanical system connected to the rotor, and the resulting speed  $\omega_m$  can be obtained from the equation

$$\frac{d\omega_m}{dt} = \frac{T_{em} - T_L}{J_{eq}} \Rightarrow \omega_m(t) = \omega_m(0) + \frac{1}{J_{eq}} \int_0^t (T_{em} - T_L) \cdot d\tau$$

where  $J_{eq}$  is the combined motor-load inertia and  $T_L$  is the load torque, which may include friction.

The rotor position  $\theta_m(t)$  is,


$$\theta_m(t) = \theta_m(0) + \int_0^t \omega_m(\tau) \cdot d\tau$$

CAPITAL THINKING.  
GLOBALLY MINDED.  
MAI I TE IHO KI TE PAE



8
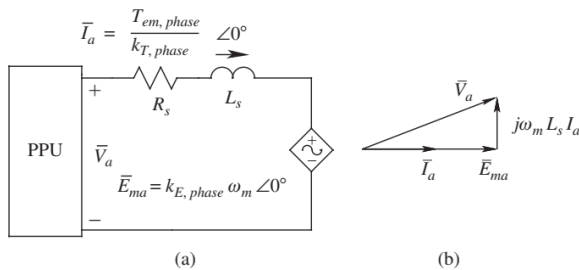
## PERMANENT-MAGNET AC MACHINES – Equivalent Circuit



In the ac steady state, using phasors, the current  $I_a$  is ensured by the feedback control to be in phase with the phase-a induced voltage  $E_{ma}$ .

The phase currents produce the total electromagnetic torque necessary to rotate the mechanical load at a speed  $\omega_m$ .

The induced back-emf  $E_{ma} = E_{rms} \angle 0^\circ$ , whose rms magnitude is linearly proportional to the speed of rotation  $\omega_m$ , is represented by a dependent voltage-source.

The applied voltage  $V_a$  in Figure **a** overcomes the back-emf  $E_{ma}$  and causes the current  $I_a$  to flow. The frequency of the phasors in Hz equals  $\omega_m/(2\pi)$  in a 2-pole PMAC machines.


There is a voltage drop across both the per-phase stator winding resistance  $R_s$  (neglected here) and a per-phase inductance  $L_s$ , which is the sum of the leakage inductance  $L_\sigma$  caused by the leakage flux of the stator winding, and  $L_m$  due to the effect of the combined flux produced by the currents flowing in the stator phases.

CAPITAL THINKING.  
GLOBALLY MINDED.  
MAI I TE IHO KI TE PAE




9


PMAC Torque-Speed Characteristics

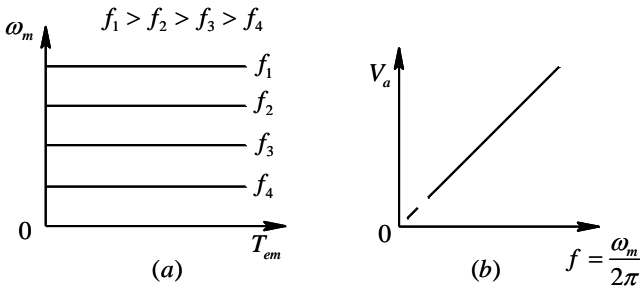

Induction Machines

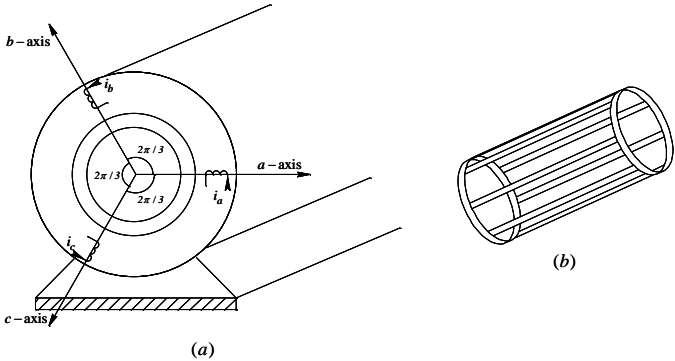
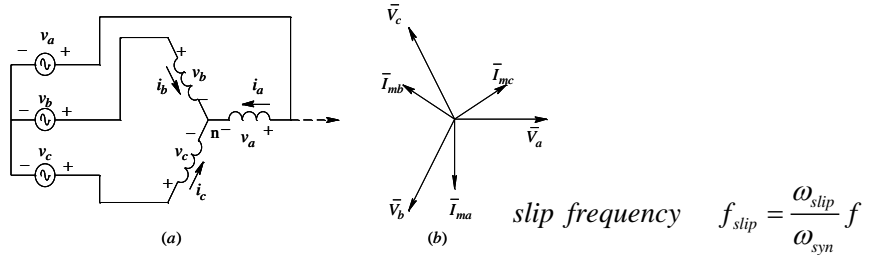
## Principles of Induction Motor Operation



$$\bar{V}_a = V_{rms} \angle 0^\circ, \quad \bar{V}_b = V_{rms} \angle -120^\circ, \quad \text{and} \quad \bar{V}_c = V_{rms} \angle -240^\circ$$

$$\bar{I}_{ma} = I_m \angle -90^\circ, \quad \bar{I}_{mb} = I_m \angle -210^\circ, \quad \text{and} \quad \bar{I}_{mc} = I_m \angle -330^\circ$$

$$\omega_{syn} = 2\pi f \quad \omega_{syn} = \frac{2\pi f}{p/2} \quad \text{for a } p\text{-pole machine}$$


$$\text{slip speed} \quad \omega_{slip} = \omega_{syn} - \omega_m$$

CAPITAL THINKING.  
GLOBALLY MINDED.  
MAI I TE IHO KI TE PAE



12

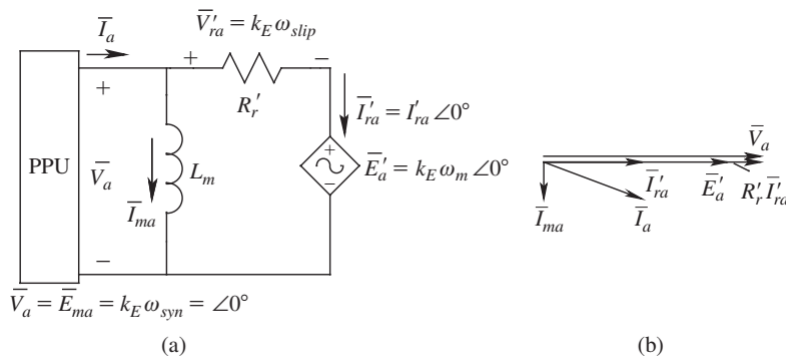
## Principles of Induction Motor Operation – Equivalent Circuit




CAPITAL THINKING.  
GLOBALLY MINDED.  
MAI I TE IHO KI TE PAE



13

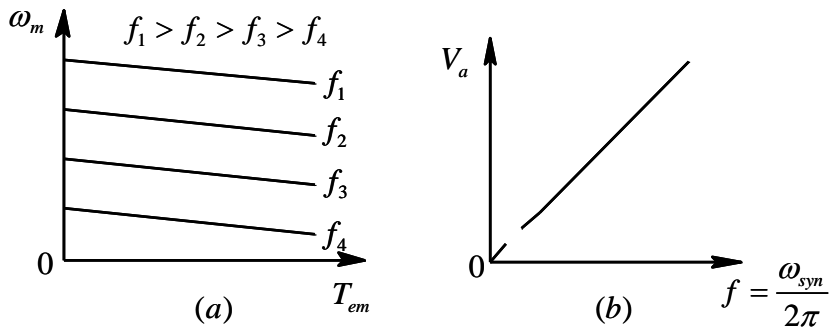


UNINTERRUPTIBLE POWER SUPPLIES (UPS)

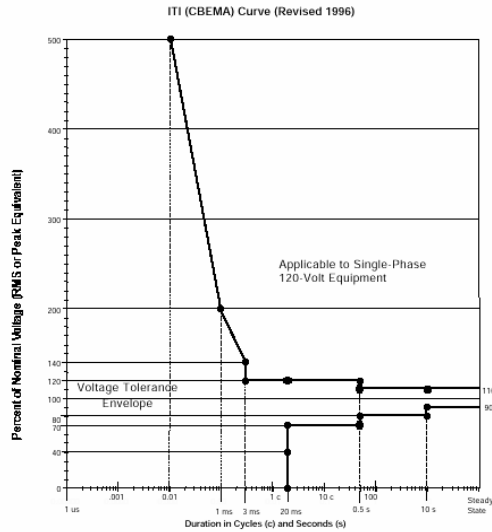

CBEMA Curve

## UNINTERRUPTIBLE POWER SUPPLIES (UPS)

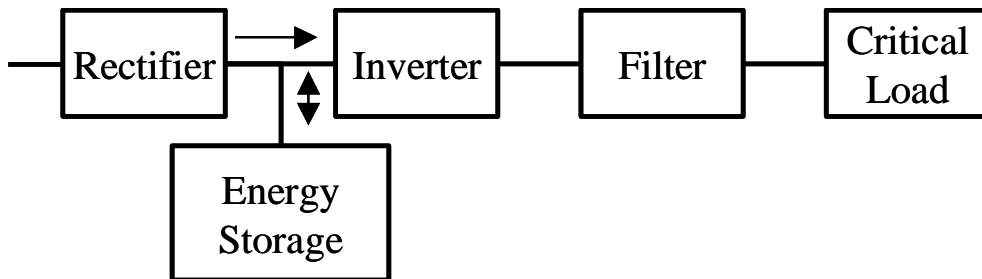

## Summary

- Converter Voltage and Current Ratings in
  - Electric Drives
  - UPS